

EECS16A DIS6B

OH: 10 AM - 12 PM PST

email: moseswon@berkeley.edu

[1] How was the MT?

[2] First Circuits discussion!

Learning Objectives

① Identify nodes and branches

② Use NVA to analyze circuit behavior

① Skill: labeling circuits

② Skill: write element voltages in terms of node voltages

③ Skill: apply KCL to circuits

④ Goal: Setup and solve a system of equations with the unknowns being node voltages

③ If time: more KVL + KCL practice

① How to identify loops for KVL equations

Today's tracklist

① Wings of liberty - Himmel

② Human Bloom - Capillary

↳ Suggested by Yoni Elisips

③ Lianne La Havas

Unstoppable

Suggest more tracks @


bit.ly/16ajukebox

EECS 16A Designing Information Devices and Systems I

Fall 2020 Discussion 6B

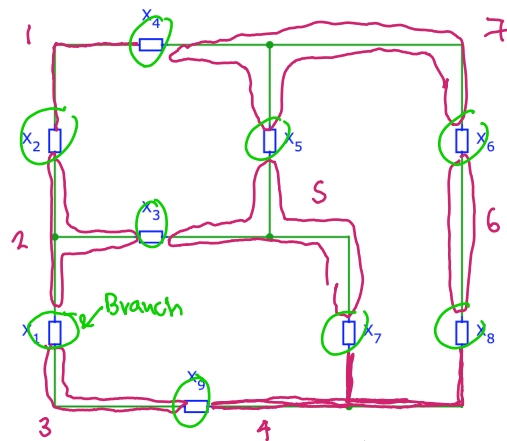1. Nodes and Branches

In the circuit shown below, label and count all nodes and branches.



Nodes: continuous piece of wire (—, $\angle$), take your pencil and draw without lifting your pencil


Branches: connections between nodes examples
→ circuit elements ($\frac{1}{2}$, $\oplus$, $\otimes$, ϕ , $\uparrow$)

→ Element currents / Branch currents - currents through a branch/element $I = 1A$

ways we
label



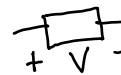→ Element voltages / Branch voltage - voltage over/across/on a branch/element



← labeling of a branch voltage

→ Node voltage - voltage on a node



Q: Does +/- direction matter?

A: In a way, we'll see

There is a really important relationship between node voltages $\neq$ element/branch voltages

2. Voltage Divider


For the circuit below, your goal will be to find the voltage V_{out} in terms of the resistances R_1 , R_2 , and V_s , using NVA (Node Voltage Analysis). The labeling steps (steps 1-4) have already been done for you.

Element voltages: $V_{R_1}, V_{R_2}, V_{out}, V_{V_s}$

Element currents: I_{R_1}, I_{R_2}, I_s

Node voltages: u_1, u_2

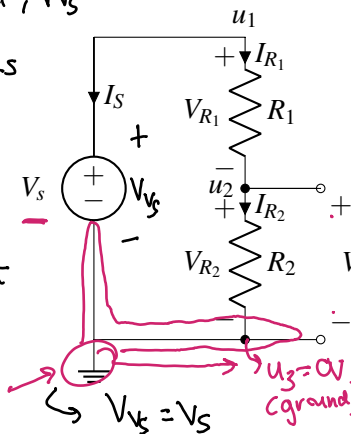NVA: The algorithm by which you find/solve for all node voltages in a circuit
↳ (unknowns)



Every element has an associated
→ element voltage

→ element current

Q: What is the relationship between node voltage & element voltage

A: element voltage = node voltage on plus end - node voltage on minus end

$$V = u_1 - u_2$$

Here is a reminder of the labeling steps followed to get the circuit diagram above:

- **Step 1:** Select a reference (ground) node. Any node can be chosen for this purpose. We will measure all of the voltages in the rest of the circuit relative to this point.
- **Step 2:** Label all nodes with voltage set by voltage sources.
- **Step 3:** Label remaining nodes.
- **Step 4:** Label element voltages and currents, following **Passive Sign Convention** (discussed below).



(polarity - plus/minus (labeling))

$$\begin{matrix} + & - \\ \text{---} & \text{---} \\ - & + \end{matrix}$$


Passive sign convention

The **passive sign convention** dictates that positive current should *enter* the positive terminal and *exit* the negative terminal of an element. Below is an example for a resistor:

↳ end/side of element

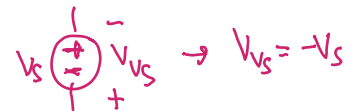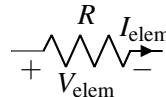

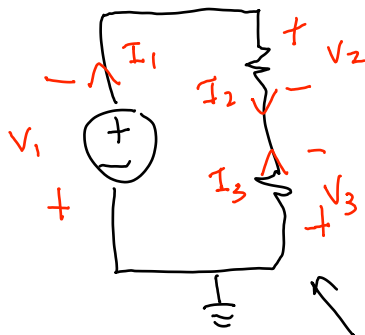
As long as this convention is followed consistently, it does not matter which direction you arbitrarily assigned each element current to; the voltage referencing will work out to determine the correct final sign. When we discuss *power* later in the module, you will see why we call this convention “passive.”




if my ground is in the same place
 $\Rightarrow$ my node voltages will be the same

To achieve your goal of **finding** V_{out} , perform the rest of the NVA steps in the boxes below:

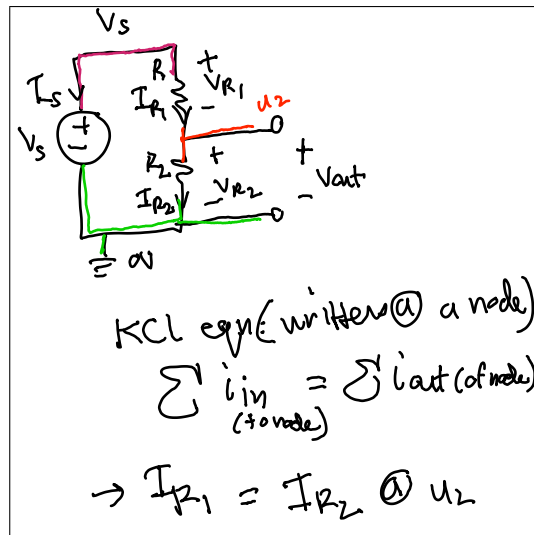
Step 5: Write KCL equations for all nodes with unknown voltages.



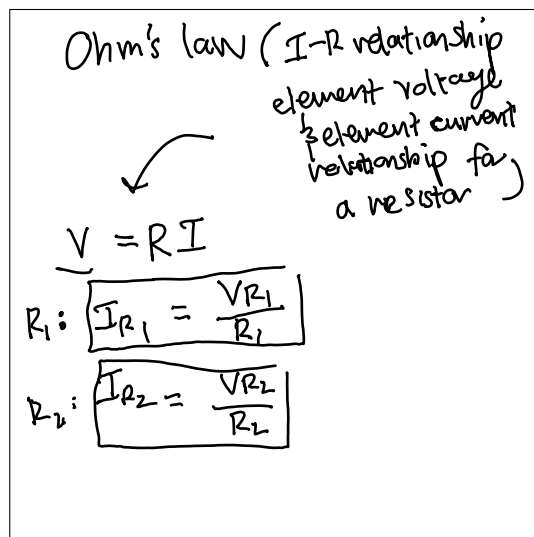Step 6: Find expressions for all element currents in terms of element voltages and characteristics.



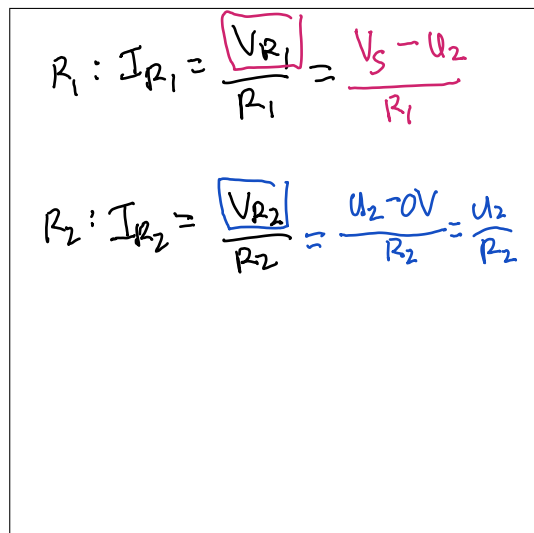Step 7: Substitute all element voltages with node voltages found in your step 6 equations.



Step 8: Substitute expressions found in step 7 into the KCL equations from step 5.

$$I_R = I_{R2}$$

$$I_R = \frac{V_S - u_2}{R_1}$$

$$I_{R2} = \frac{u_2}{R_2}$$

$$\frac{V_S - u_2}{R_1} = \frac{u_2}{R_2} \quad \checkmark$$

Step 9: Solve for the node voltage values. At this point the analysis procedure is effectively complete - all that's left to do is solve the system of linear equations (by applying Gaussian Elimination, inverting $\mathbf{A}$, etc.) to find the values for the u 's. Then we can go back to our Step 7 equations and calculate the I 's. Note that in our circuit, $V_{out} = u_2 - 0 = u_2$.

1 eqn
1 unk. (u_2)

skipping algebra

$$u_2 = \frac{R_2}{R_1 + R_2} V_S$$

Q: ~~W~~ Can we choose $\dagger$ - labelings separately for each element?
Yes! The labeling on R_1 doesn't affect labeling on R_2

Q: What direction is the current moving in, in the real physical system:


A: Assume
 $V_s > 0$



Extra notes:




Terms you might hear or read: "solve a circuit" - meaning: find all quantities (element voltages + element currents) in terms of component values (e.g. resistances, voltage sources, current sources)

Examples of passive sign convention

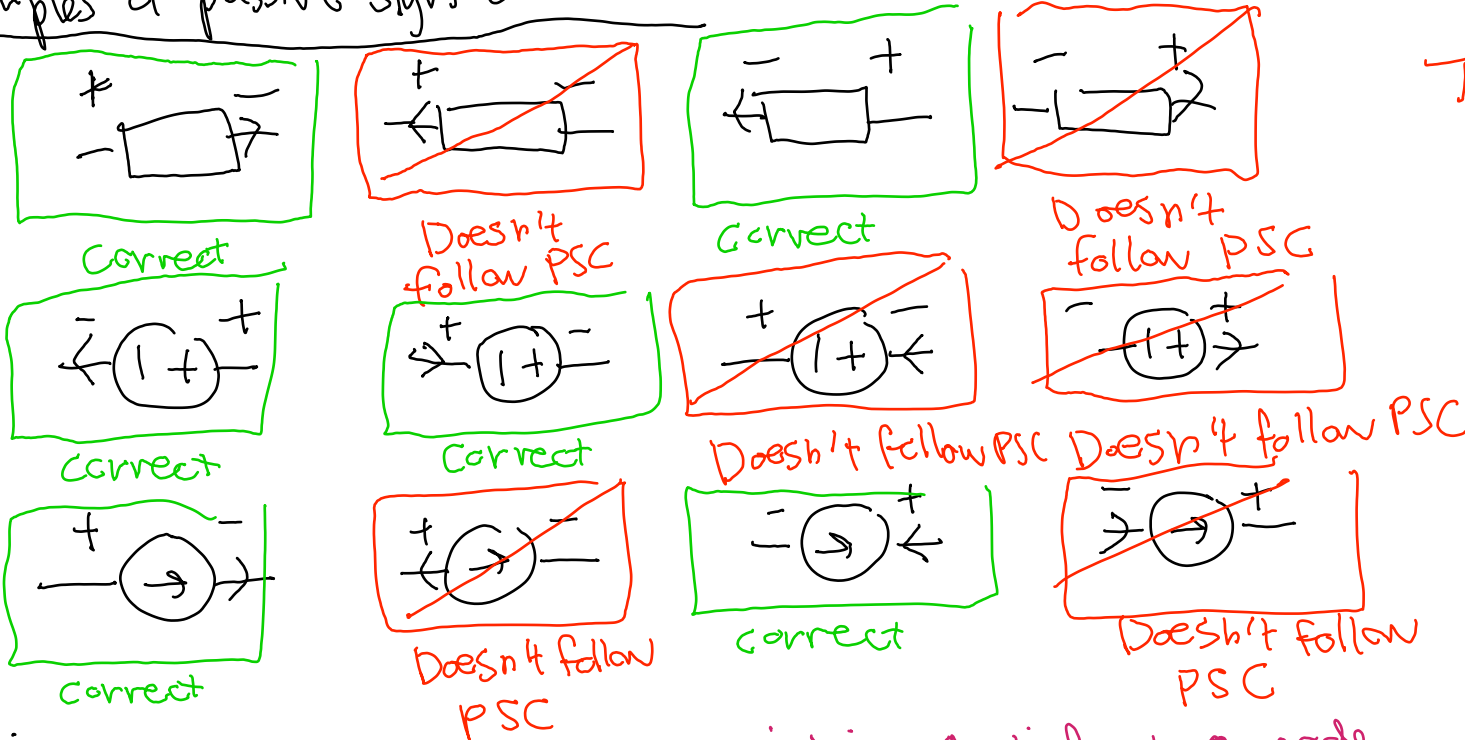

The ones that fail have a mismatch between $\vec{i}$ (current direction) & $+$ $-$ (voltage polarity)

Applying KCL examples

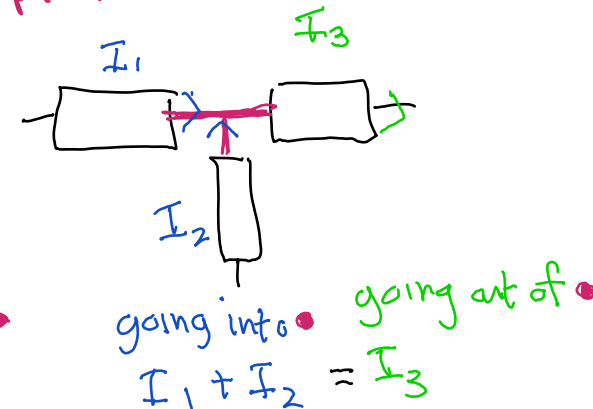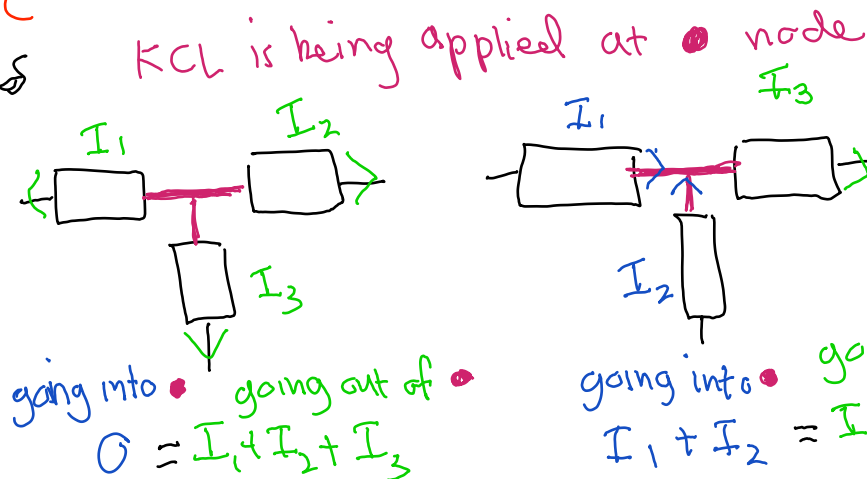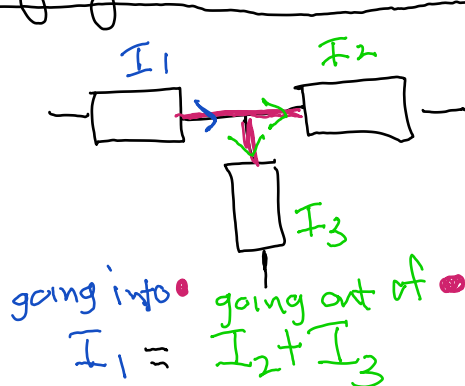


KCL equation depends on how currents are oriented

3. Practice: A Simple Circuit

Use KVL and/or KCL to solve the following circuits.

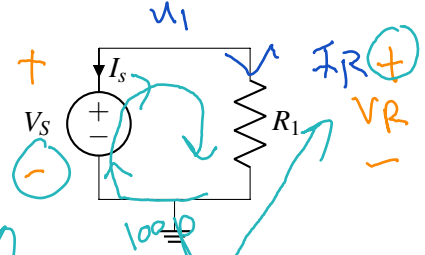- (a) For this problem assume $V_S = 1V$ and $R_1 = 1k\Omega$. Find the current, I_S flowing through the voltage source.



Writing KVL

- Start at some node (ground in this case)
- Go through an element signing each element voltage with the first sign you hit.

KCL @ top node:

$$I_S + I_R = 0$$

$$I_S = -I_R$$

KVL around loop:

$$-V_S + V_R = 0$$

$$V_R = V_S$$

Ohm's law:

$$V_R = R I_R \Rightarrow I_R = \frac{V_R}{R}$$


$$I_S = -\frac{V_S}{R} = -\frac{5V}{1k\Omega} = -1mA$$

($kilo = 1000$, $milli = \frac{1}{1000}$)

$\frac{V}{\Omega} = A$

Negative means current in system goes in opposite direction to what was labeled. A positive 1mA goes up.

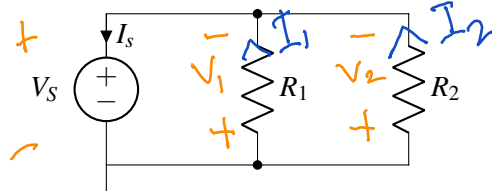- (b) For this problem assume $V_S = 1V$, $R_1 = 2k\Omega$, and $R_2 = 2k\Omega$. Find the current, I_S flowing through the voltage source.



KVL loop 1

$$-V_S - V_1 = 0$$

$$V_1 = -V_S$$

KVL loop 2

$$-V_S - V_2 = 0$$

$$V_2 = -V_S$$

KCL @ top node

$$I_S = I_1 + I_2$$

Ohm's law

$$\frac{V_1}{R_1} = I_1, \frac{V_2}{R_2} = I_2$$

$$I_S = -\frac{V_S}{R_1} - \frac{V_S}{R_2}$$

$$I_S = -\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_S$$

$$I_S = -\left(\frac{1}{2k\Omega} + \frac{1}{2k\Omega}\right)1V$$

$$I_S = -1mA$$