

EECS16A DIS 8A

Learning Objectives

① Modeling 2-D touch screen designs (translating physical system to circuit)

① Review of what was in lecture / note 14

② New alternative design

② Resistor equivalence practice

① Identifying series

② Identifying parallel

③ Voltages and currents in series and parallel

Today's playlist

① Alone - Miso

② Hi High - LOONA

③ Any Song - ZICO

Suggest @

bit.ly/16ajukebox

Other announcements

① Review sessions

② Welcome,






Ashwin + Dahlia's
students

③ Korinna (ASE)
will be helping out

email: moseswan@

wednesday




HWP: 10AM-12PM PST

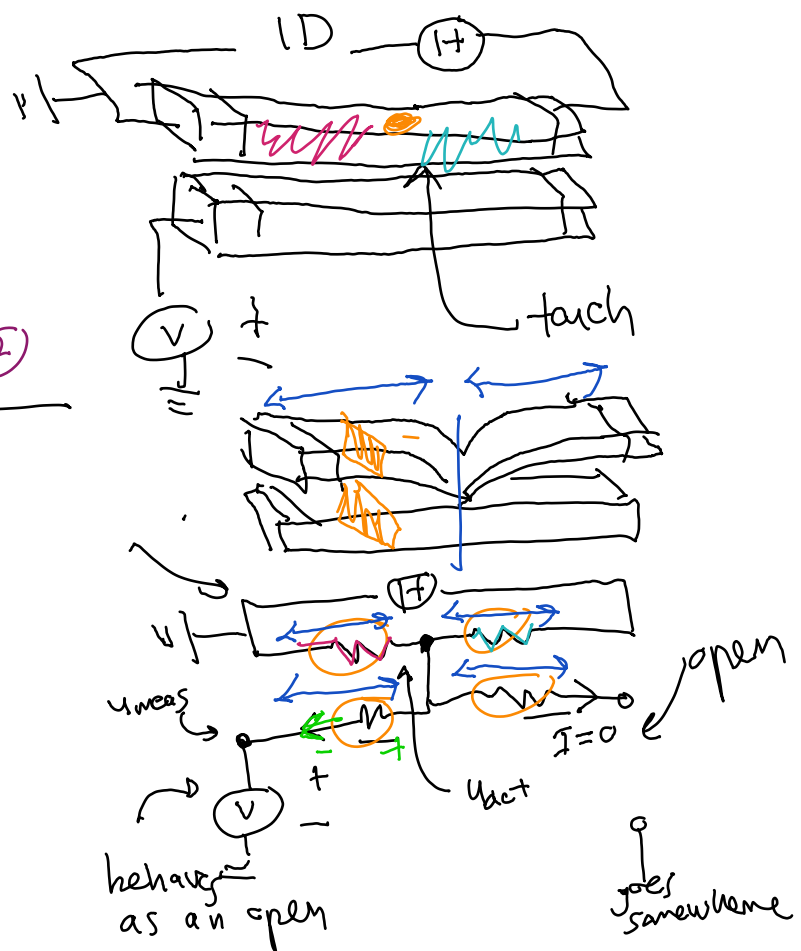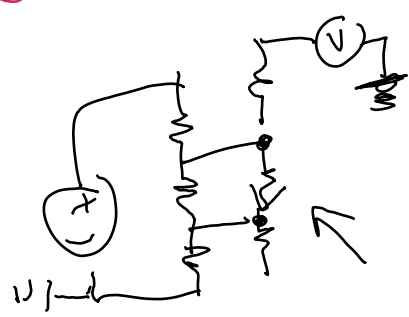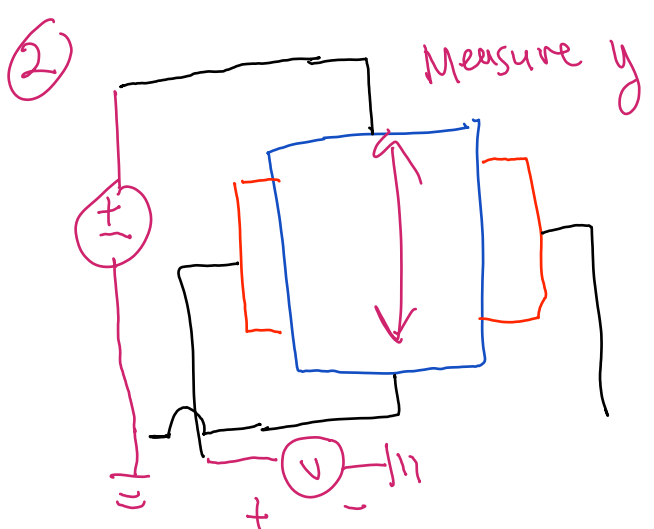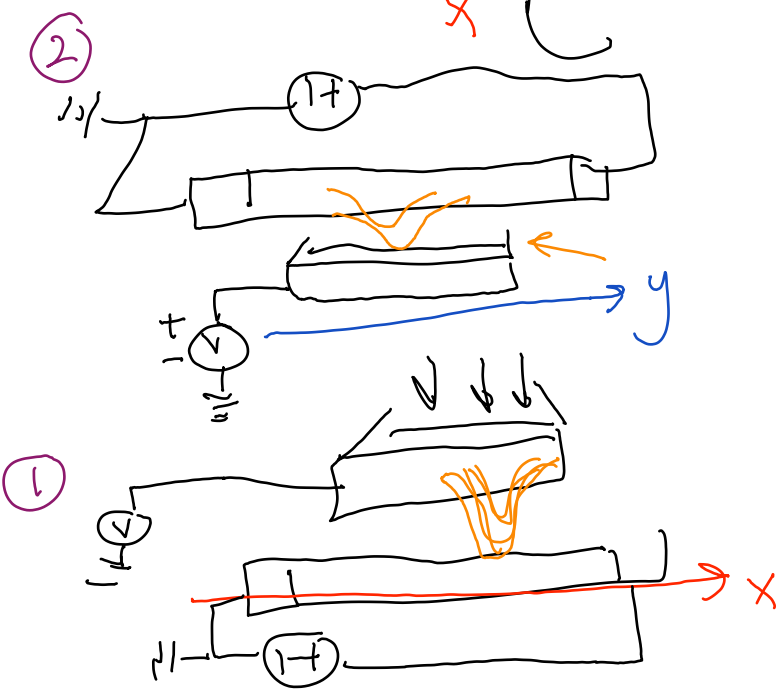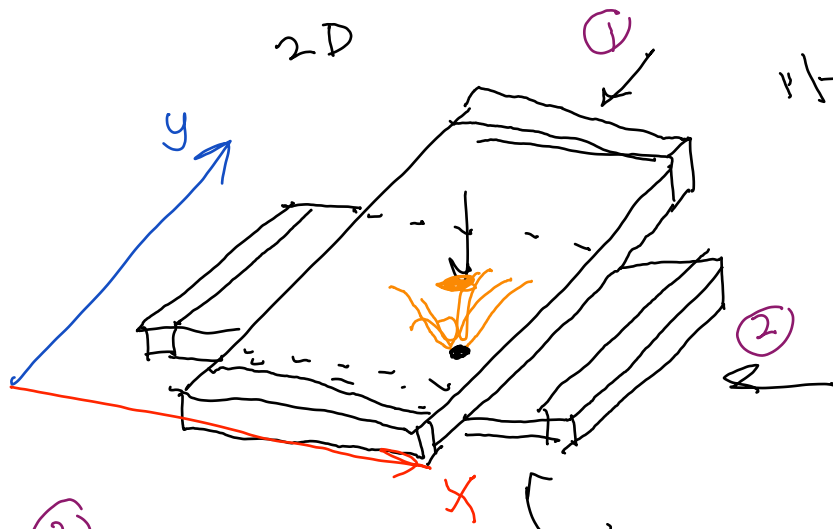


$$U_{act} - U_{meas} = IR$$

$$= 0 \quad (I=0)$$

$$U_{act} = U_{meas}$$

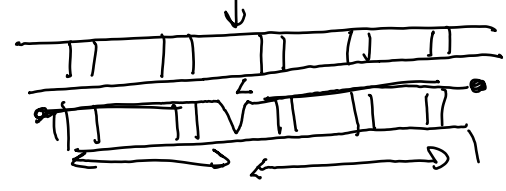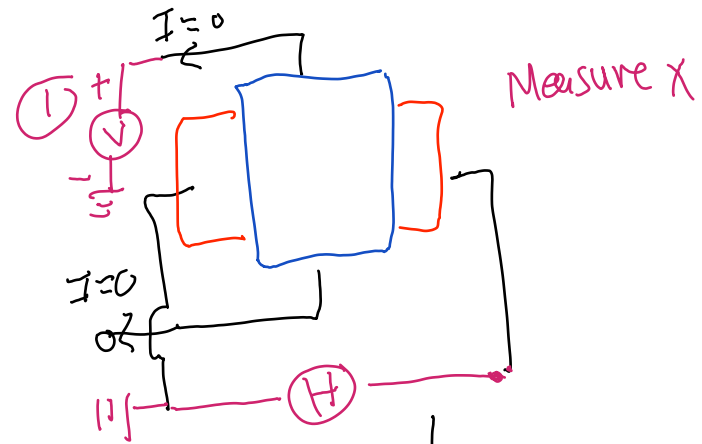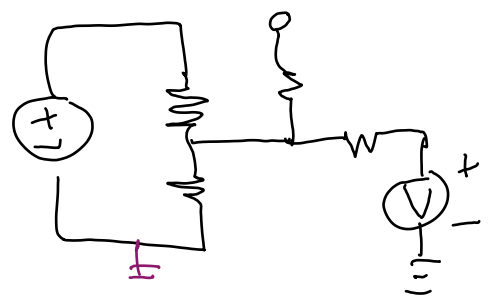

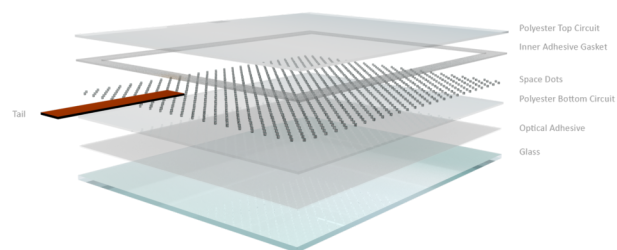







EECS 16A Designing Information Devices and Systems I Discussion 8A

1. Resist the Touch

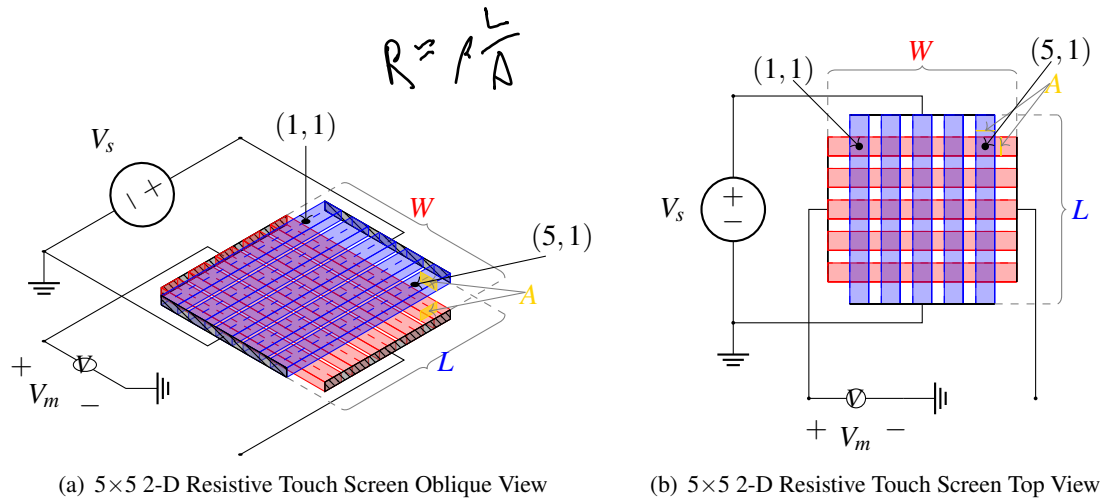



Figure 1: $N \times N$ Resistive Touch Screen, $N = 5$


In this question we will be re-examining the 2-dimensional resistive touchscreen. This touchscreen, is slightly different to the one shown in lecture and more like the one we will be examining in lab.

The touchscreen has length L and width W and is composed of a rigid bottom-layer and a flexible top-layer. Instead of having two continuous resistive sheets on the top and bottom layers, this is a simpler implementation with N vertical strips of conductive material in the top layer and N horizontal strips of conductive material in the bottom layer. The strips of a single layer are all connected by an ideal conducting plate on each side. All strips have resistivity, ρ , and cross-sectional area, A .

Assume that all top layer resistive strips and bottom layer resistive strips are spaced apart equally, and that the upper left touch point in Figure 1(b) is position $(1,1)$, and the upper right touch point is $(N,1)$. The spacing between the strips in the top layer is $\frac{W}{N+1}$, and the spacing between the strips in the bottom layer is $\frac{L}{N+1}$.

- (a) Find the resistance R_y for a single vertical blue strip and R_x for a single horizontal red strip, as a function of the screen dimensions W and L , the strip resistivity ρ , and the cross-sectional area A .

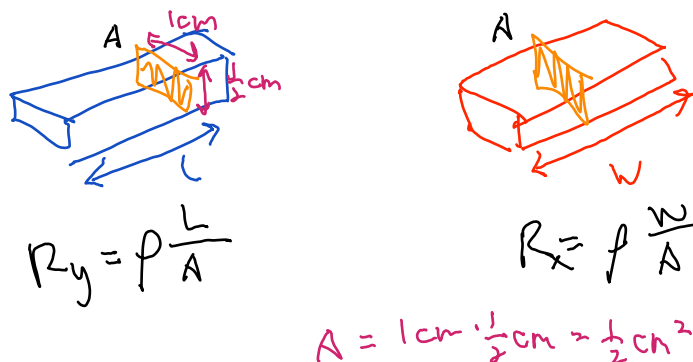

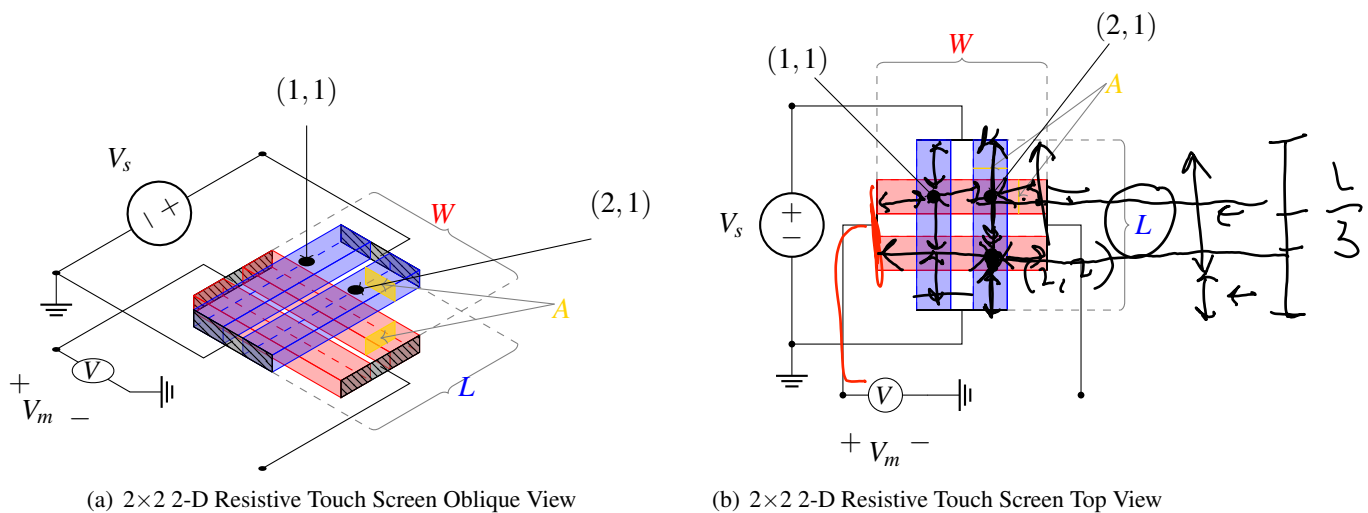
Figure 2: 2×2 Resistive Touch Screen

(b) Consider a 2×2 example for the touchscreen circuit, shown in Figure 2.

Assume that we connect a voltage source V_s , between the top and bottom terminals of the blue strips, and a voltmeter V_m to one of the left or right terminals as depicted in the diagram.


If $V_s = 3\text{ V}$, $R_x = 2000\Omega$, and $R_y = 2000\Omega$, draw the equivalent circuit for when the point $(2,2)$ is pressed and solve for the measured voltage, V_m , with respect to ground.

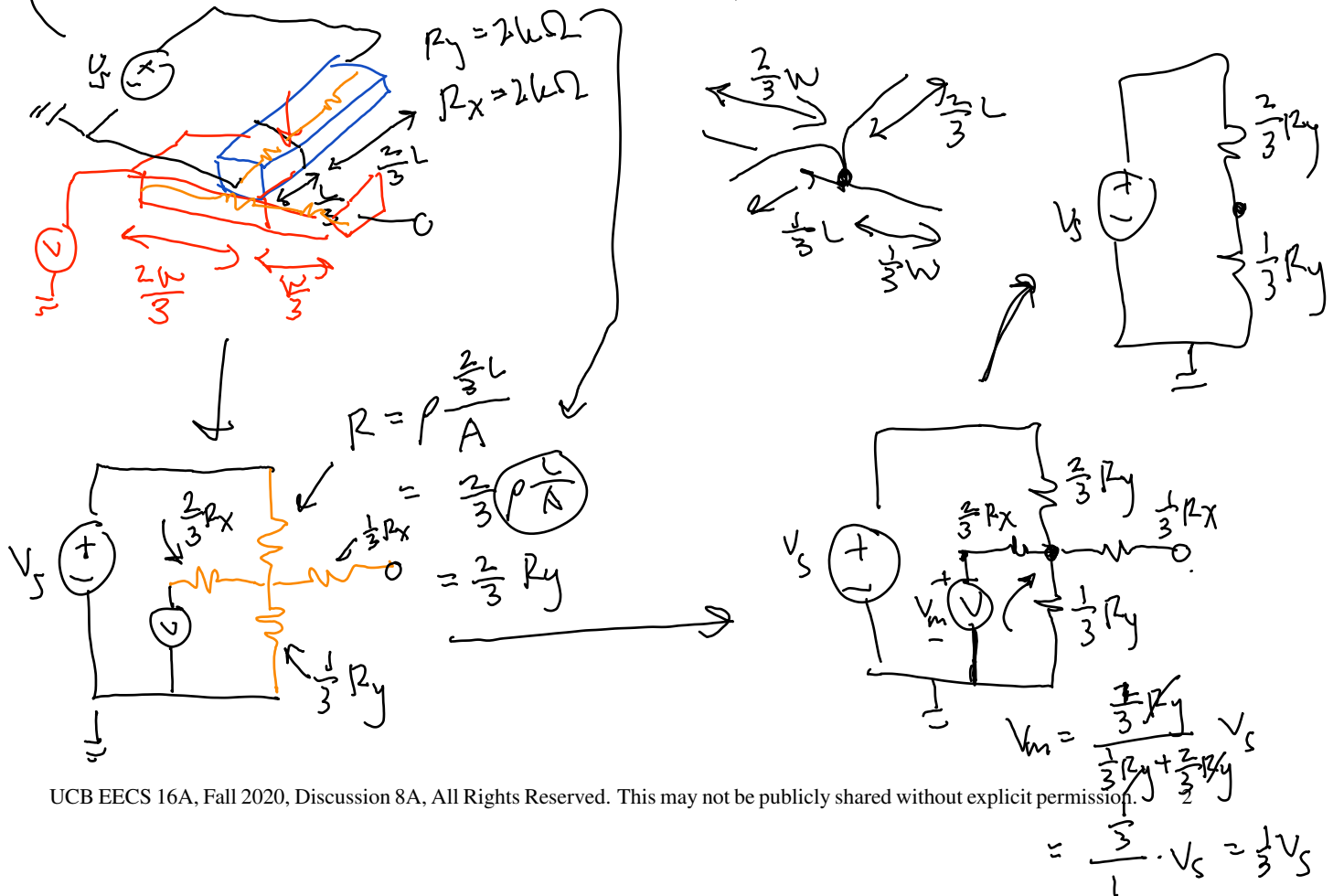Reminder: all top layer resistive strips and bottom layer resistive strips are spaced apart equally, and that the upper left touch point is position $(1,1)$. The spacing between the strips in the top layer is $\frac{W}{N+1}$, and the spacing between the strips in the bottom layer is $\frac{L}{N+1}$.




One thing that we didn't model above is the top left blue bar and the bottom top red bar.

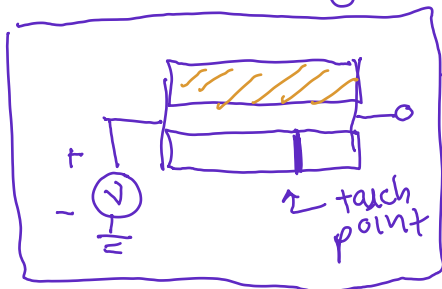
This is the way it would appear in the diagram




height:
lower

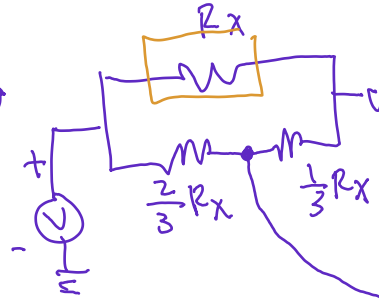

Touch point

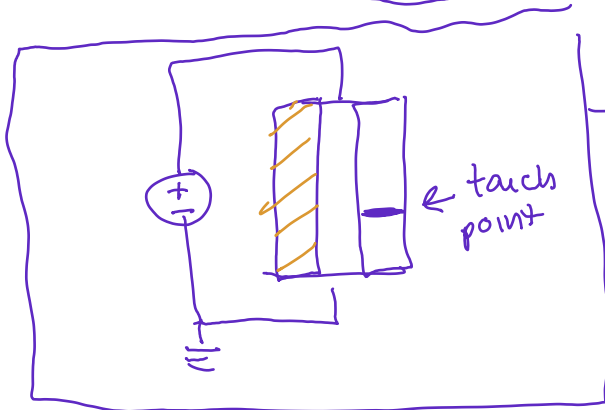


height:
higher

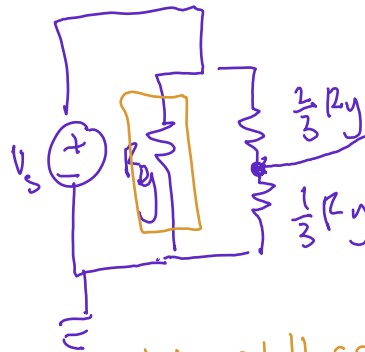


The added bars don't matter. We still see V_s over both R_y and the $\frac{2}{3}R_y + \frac{1}{3}R_y$, and no current goes through the R_x .

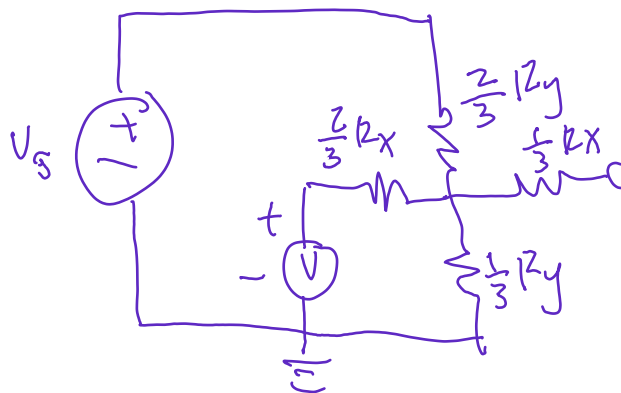Also, note, our circuit is only setup to measure y right now. If we drop the R_x and R_y that isn't affecting us, we simply have what was shown on the previous page,



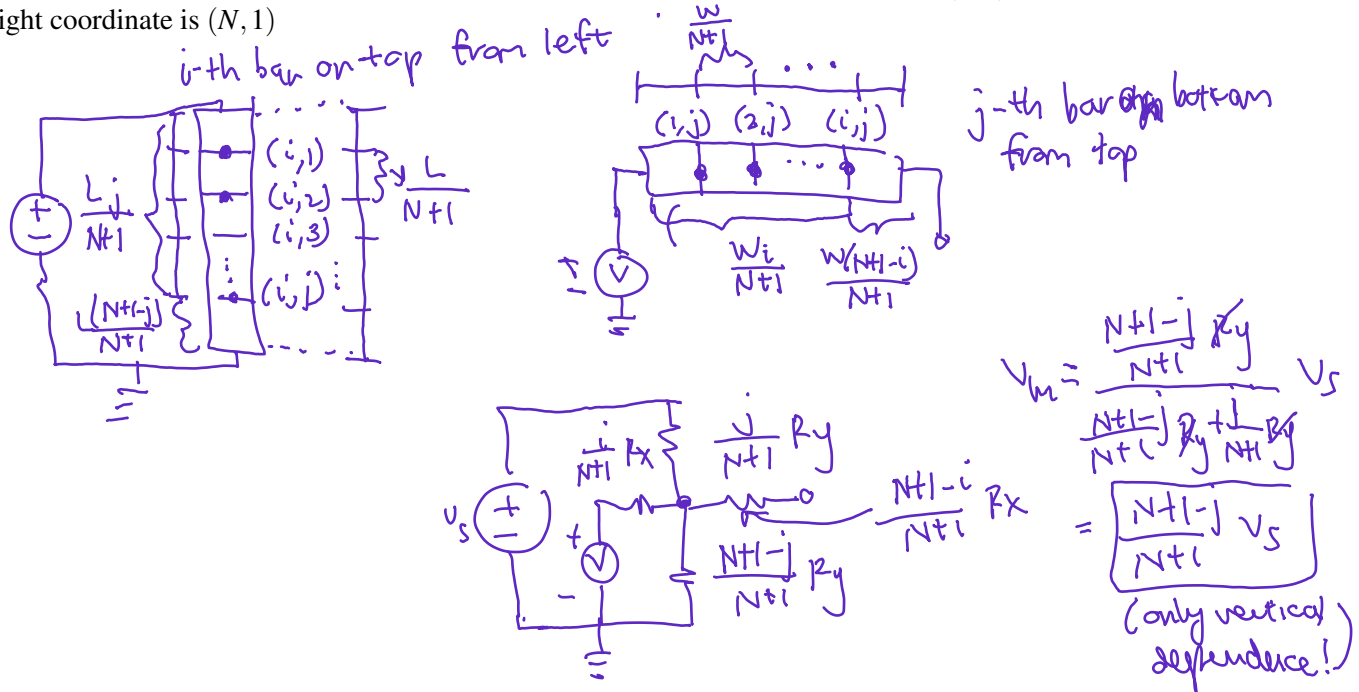- (c) Suppose a touch occurs at coordinates (i, j) for an arbitrary $N \times N$ touchscreen, and the voltage source and meter are connected as in the figures. A 5×5 example is shown in Figure 1(b). Find an expression for V_m as a function of V_s , N , i , and j . Again, the upper left corner is the coordinate $(1, 1)$ and the upper right coordinate is $(N, 1)$



- (d) Optional / Fun: Experiment with the TinkerCad models below to validate the theoretical results you just derived.

TinkerCad model of 2×2 equivalent circuit: <https://www.tinkercad.com/things/0wIXz3MkD7B>


TinkerCad model of 3×2 equivalent circuit: <https://www.tinkercad.com/things/k5oolj2tUEN>

Falstad + Tinkercad are great!
They can help you verify your analysis!

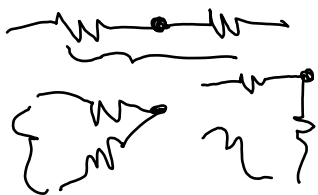2. Practice: Series and Parallel Combinations

For the resistor network shown below, find an equivalent resistance between the terminals A and B using the resistor combination rules for series and parallel resistors.

① Series: two components share a single node, nothing else on it








$$R_{eq} = R_1 + R_2$$

② Parallel: two resistors are in parallel if they share the same pair of nodes



$$R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

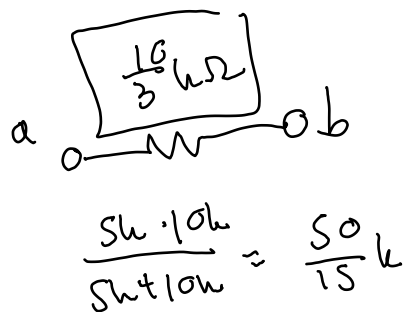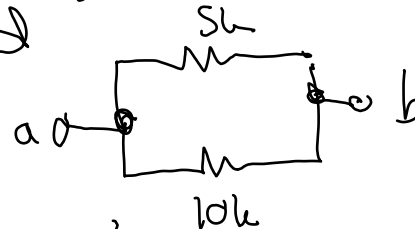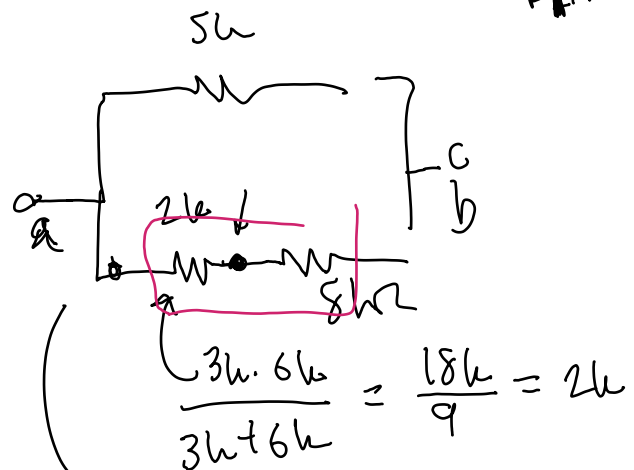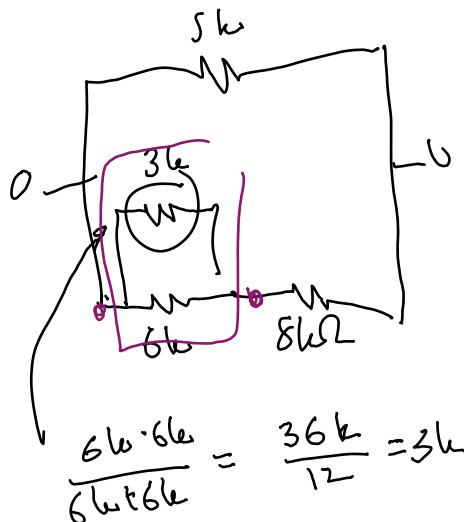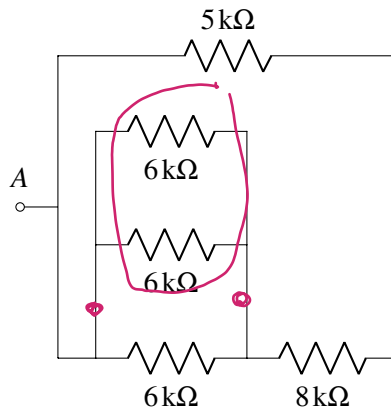

Example

