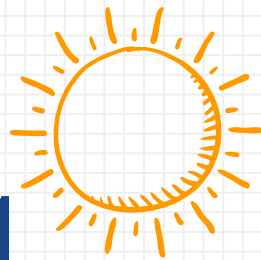


EECS16A Imaging 1



Insert your names here



Semester Outline



Imaging
Module



Touchscreen
Module



Locationing
Module

Today's Lab: Imaging Part 1

- You should have received lab materials (TI MSP430F5529 + lab kit)
- Circuits + Breadboarding 101
- Build circuit that reacts to light intensity
 - Use Launchpad/TinkerCAD to see how the circuit behaves
- Graded checkoff starts today!
- If you haven't received your lab kit yet, you can still do today's lab and get checked off





Today's Lab: Imaging Part 1

- Hardware lab
 - Uses physical Launchpad and breadboard
 - All students with kits should do this option
- Software lab
 - Uses online circuit simulations in TinkerCad
 - Look at other group members' physical setups and lab videos to get an idea of the hardware
 - All students without kits should do this option




Our circuit

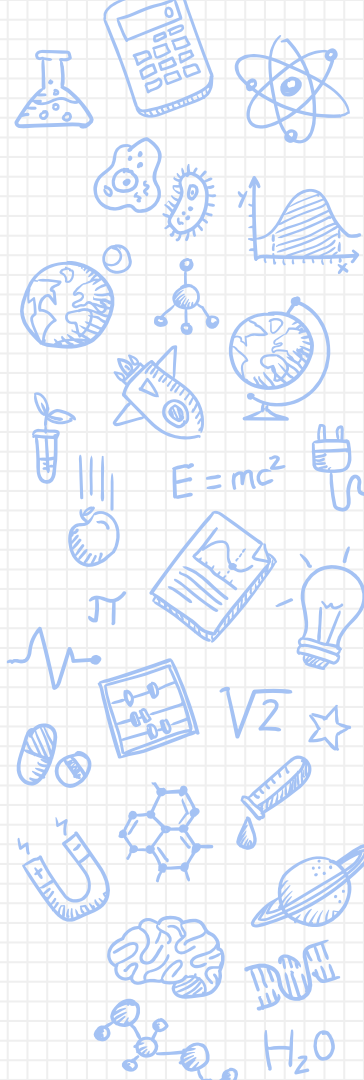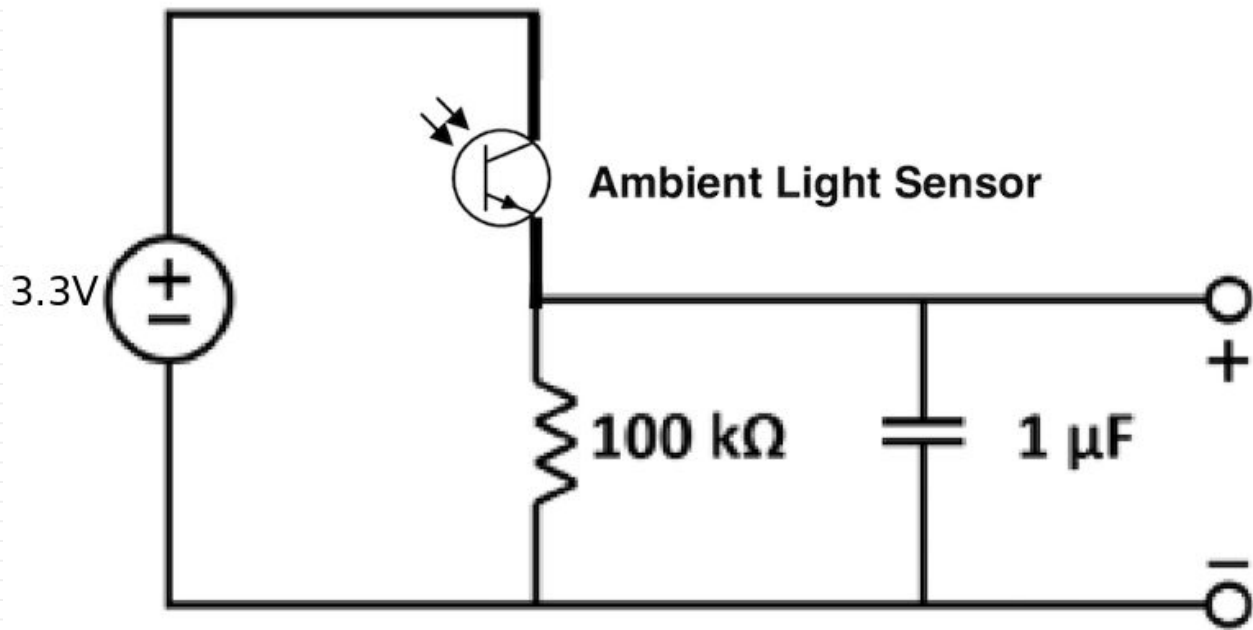

A Little Physics: Voltage, Current, and Resistors

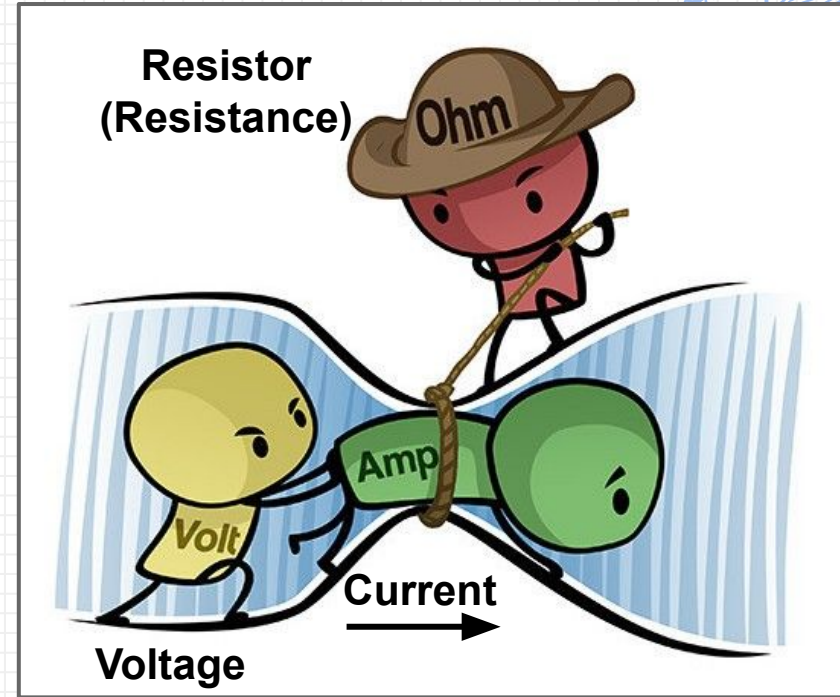- **Voltage [Volts]** - pushes charge through circuit
- **Current [Amps]** - flow of charge through circuit
 - 1 Amp = 1 charge per second
- **Resistor [Ohms]** - circuit component that resists the flow of charge through circuit







Simple Circuit: The Tools™

- **Components**
 - Resistors
 - Capacitors
 - Voltage Source
- **Wires / Jumpers [male-to-male vs male-to-female]**



What's in your circuit? : Resistors

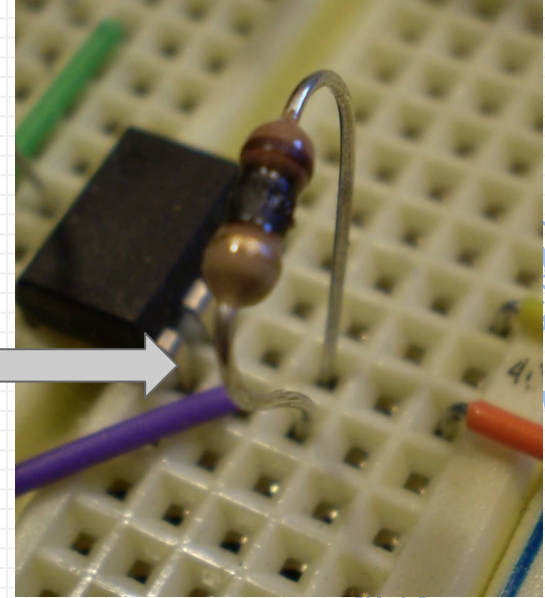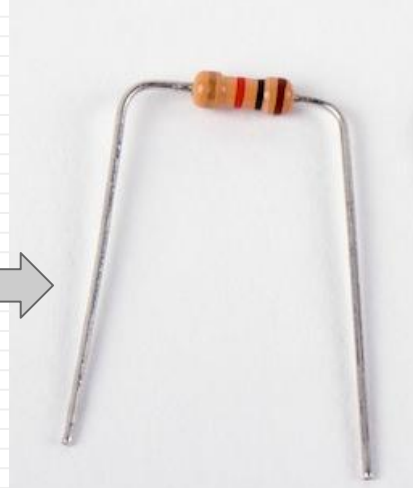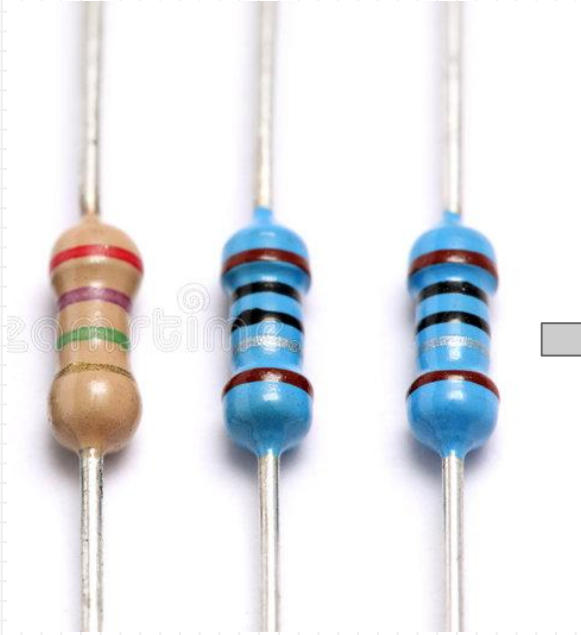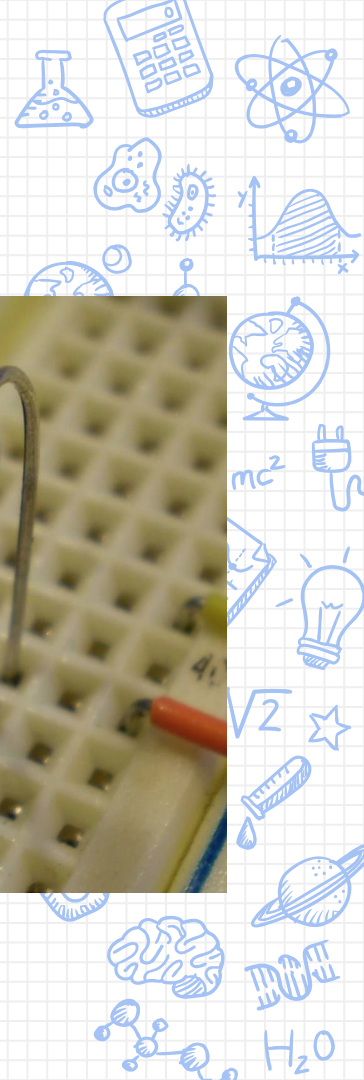


What's on your circuit? : Resistors



4 Band Resistor Color Coding



COLOR	1ST BAND	2ND BAND	MULTIPLIER	TOLERANCE
BLACK	0	0	x1 Ω	
BROWN	1	1	x10 Ω	$\pm 1\%$
RED	2	2	x100 Ω	$\pm 2\%$
ORANGE	3	3	x1000 Ω	
YELLOW	4	4	x10000 Ω	
GREEN	5	5	x100000 Ω	$\pm 0.5\%$
BLUE	6	6	x1000000 Ω	± 0.25
VIOLET	7	7	x10000000 Ω	± 0.10
GREY	8	8		± 0.05
WHITE	9	9		
GOLD			0.1	$\pm 5\%$
SILVER			0.01	$\pm 10\%$

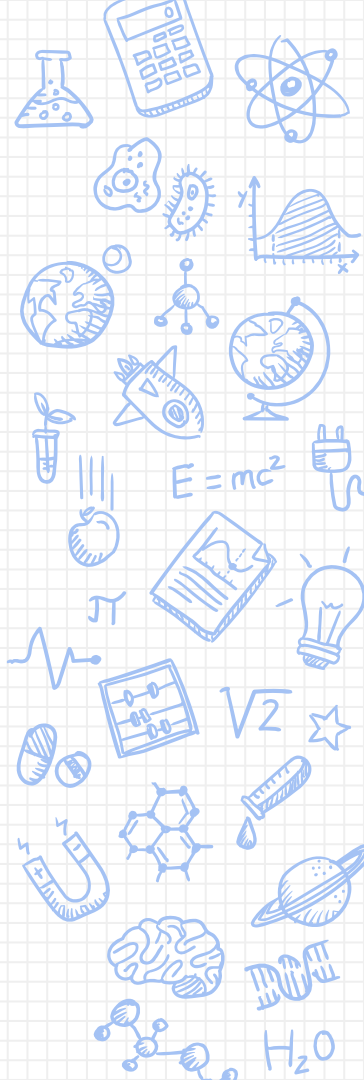

Poll Time! What color is a 100 ohm resistor?



4 Band Resistor Color Coding



COLOR	1ST BAND	2ND BAND	MULTIPLIER	TOLERANCE
BLACK	0	0	x1Ω	
BROWN	1	1	x10Ω	±1%
RED	2	2	x100Ω	±2%
ORANGE	3	3	x1000Ω	
YELLOW	4	4	x10000Ω	
GREEN	5	5	x100000Ω	±0.5%
BLUE	6	6	x1000000Ω	±0.25
VIOLET	7	7	x10000000Ω	±0.10
GREY	8	8		±0.05
WHITE	9	9		
GOLD			0.1	±5%
SILVER			0.01	±10%

1. black-brown-red
2. brown-black-brown
3. brown-black-red
4. brown-black-black

Poll Time! What color is a 100 ohm resistor?



4 Band Resistor Color Coding



COLOR	1ST BAND	2ND BAND	MULTIPLIER	TOLERANCE
BLACK	0	0	x1Ω	
BROWN	1	1	x10Ω	±1%
RED	2	2	x100Ω	±2%
ORANGE	3	3	x1000Ω	
YELLOW	4	4	x10000Ω	
GREEN	5	5	x100000Ω	±0.5%
BLUE	6	6	x1000000Ω	±0.25
VIOLET	7	7	x10000000Ω	±0.10
GREY	8	8		±0.05
WHITE	9	9		
GOLD			0.1	±5%
SILVER			0.01	±10%

1. black-brown-red
2. **brown-black-brown**
3. brown-black-red
4. brown-black-black



1. brown-black-red
2. brown-black-brown
3. brown-black-yellow
4. brown-black-white

Poll Time! What color is a 100K resistor? (100 kilo-ohms, so 100,000 ohms)



4 Band Resistor Color Coding





COLOR	1ST BAND	2ND BAND	MULTIPLIER	TOLERANCE
BLACK	0	0	x1 Ω	
BROWN	1	1	x10 Ω	$\pm 1\%$
RED	2	2	x100 Ω	$\pm 2\%$
ORANGE	3	3	x1000 Ω	
YELLOW	4	4	x10000 Ω	
GREEN	5	5	x100000 Ω	$\pm 0.5\%$
BLUE	6	6	x1000000 Ω	± 0.25
VIOLET	7	7	x10000000 Ω	± 0.10
GREY	8	8		± 0.05
WHITE	9	9		
GOLD			0.1	$\pm 5\%$
SILVER			0.01	$\pm 10\%$

1. brown-black-red
2. brown-black-brown
3. **brown-black-yellow**
4. brown-black-white

A diagram showing a wheel of radius R on a horizontal surface. A horizontal force F is applied at the center of the wheel, pointing to the right. A friction force f is shown at the contact point between the wheel and the surface, pointing to the left. The wheel is represented by a circle, and the surface by a thick horizontal line.


Equipment for Today: Capacitors

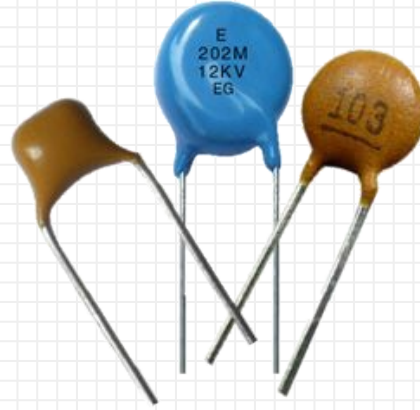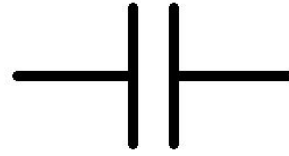


They store your charge!
Called capacitors because they
have a set capacity (in Farads)



Equipment for Today: Wires/Jumpers

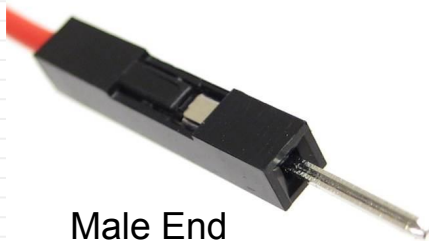

Male End


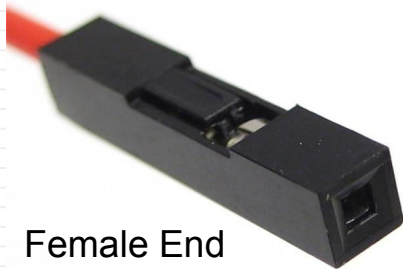


Female End




Equipment for Today: Voltage Source

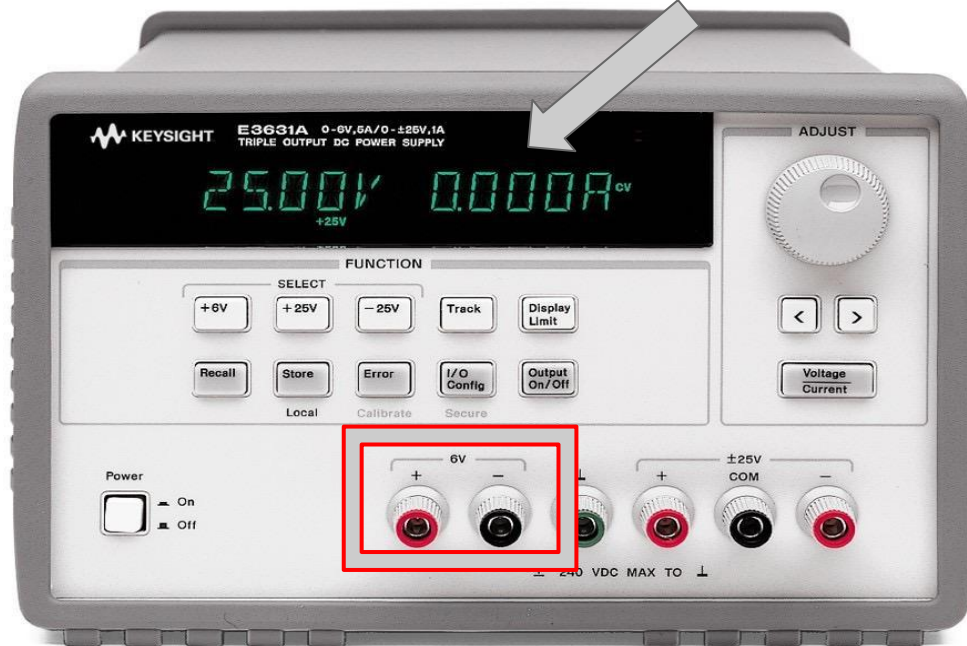
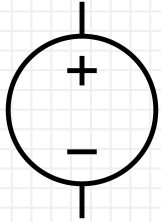
**IMPORTANT: Always keep
current limited @ 0.1 A limit**



PSU cables
are hanging
on back wall

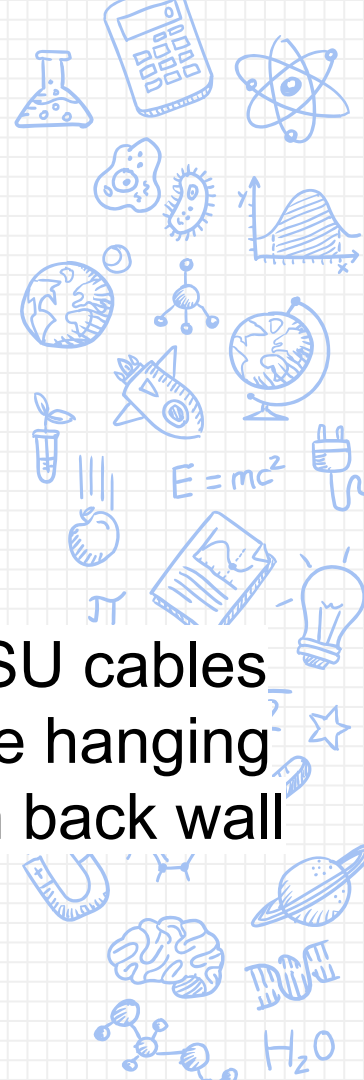


Equipment for Today: Voltage Source

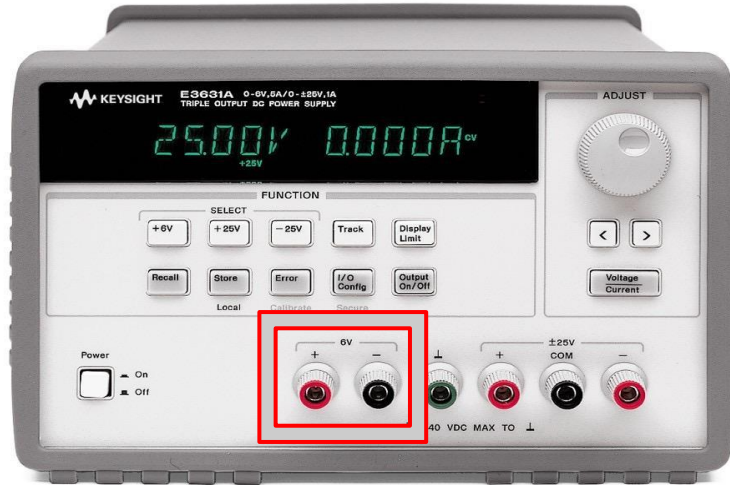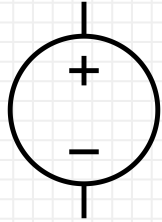

Power Supply Unit (PSU)

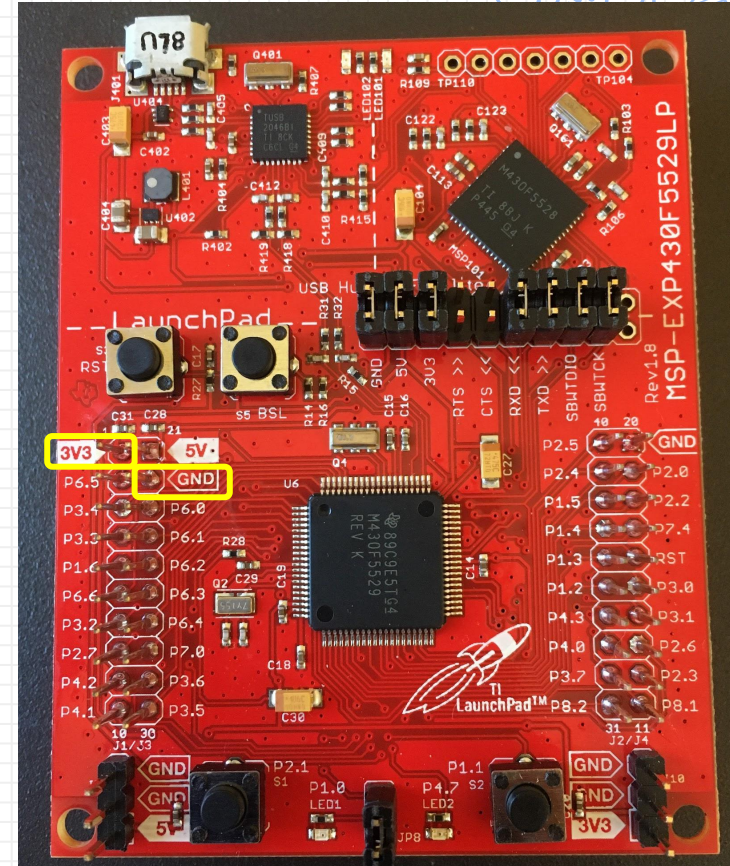We will be using the LaunchPad instead of the PSU as our voltage source. The 3V3 and GND pins on the LaunchPad are the + and - terminals of the voltage source respectively




Simple Circuit: The Theory

- Components
- Nodes
 - Point in circuit where circuit elements meet
 - Wire between components are considered part of one node
- We know you don't know much about circuits yet; we've given you very detailed instructions on how to build the circuit in the lab



Simple Circuit: The Theory™

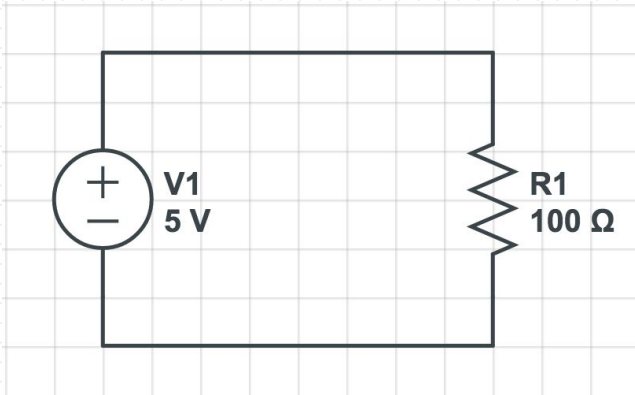- Components (Resistors, LEDs, Capacitors)
- Nodes
 - Point in circuit where circuit elements meet
 - Wire between components are considered part of one node



What components?

How many nodes?

Where are these nodes?





1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31 32 33 34 35 36 37 38 39 40 41 42 43 44 45 46 47 48 49 50 51 52 53 54 55 56 57 58 59 60 61 62 63 64 65 66 67 68 69 70 71 72 73 74 75 76 77 78 79 80 81 82 83 84 85 86 87 88 89 90 91 92 93 94 95 96 97 98 99 100






Breadboard Do's and Don't's

How do we make this circuit? →

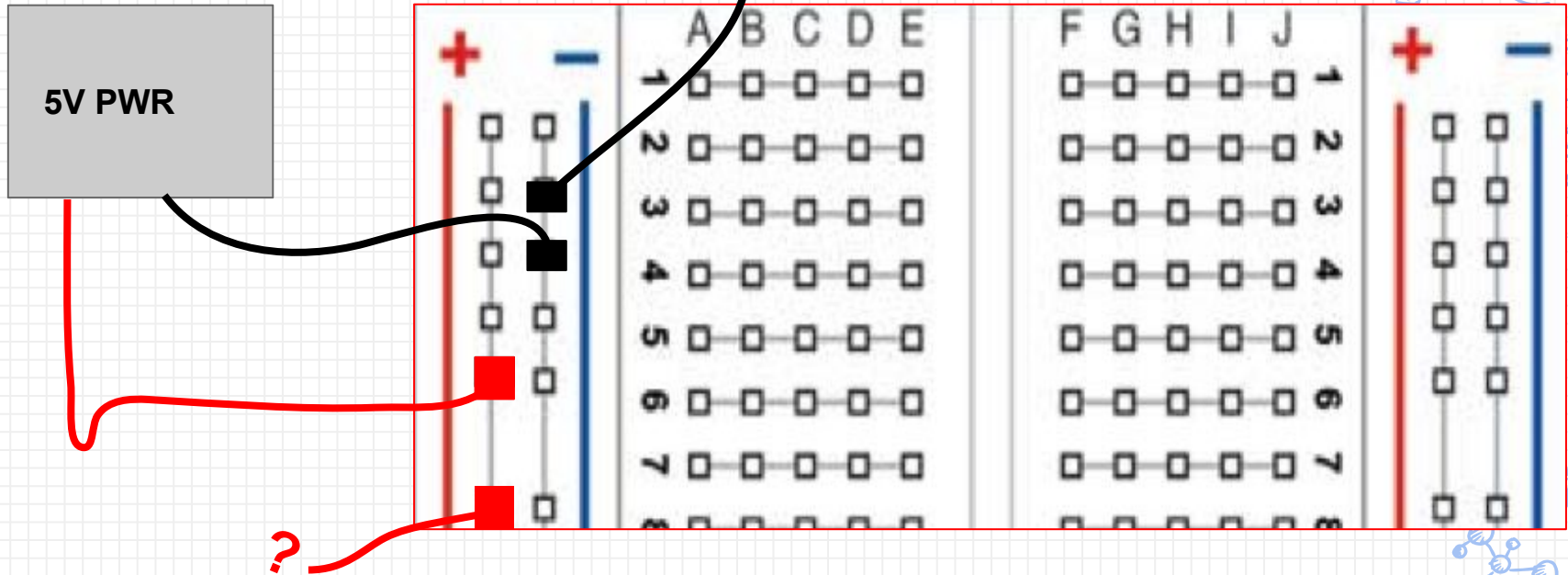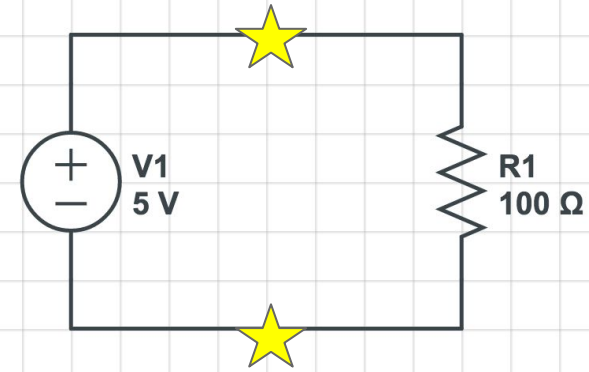




Breadboard Do's and Don't's

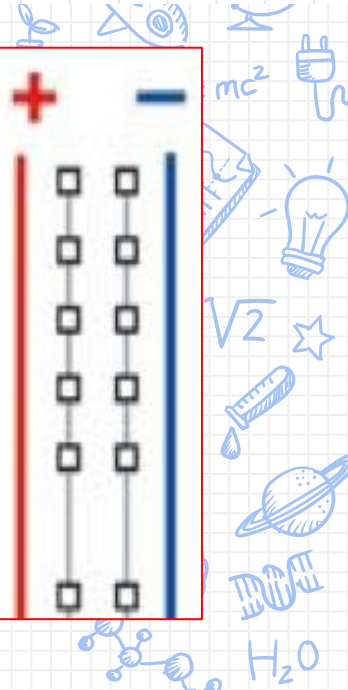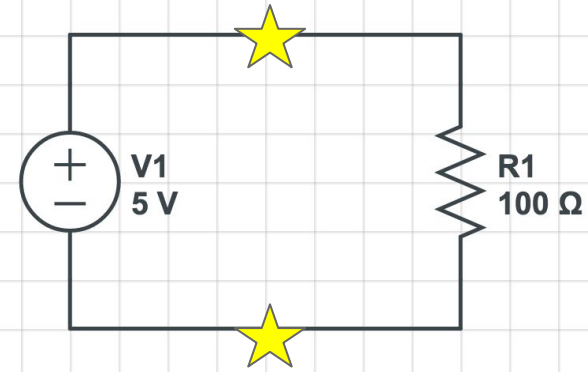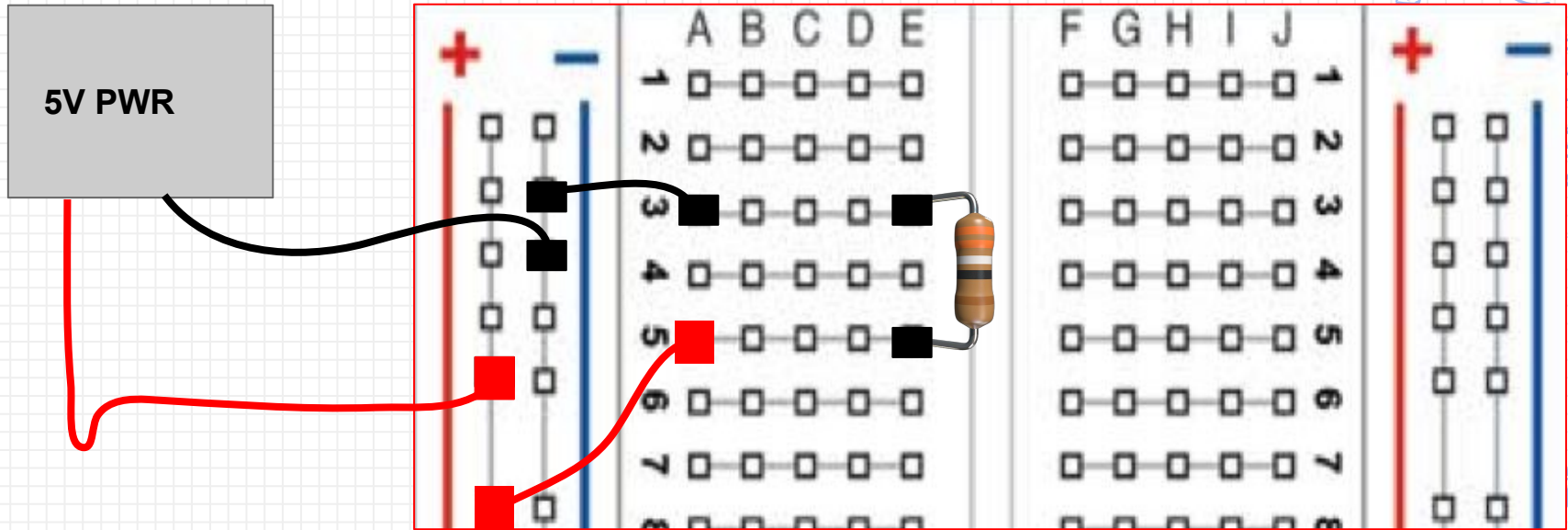- ✓ **Do** plug component's ends into two different rows - separate nodes





Breadboard Do's and Don't's

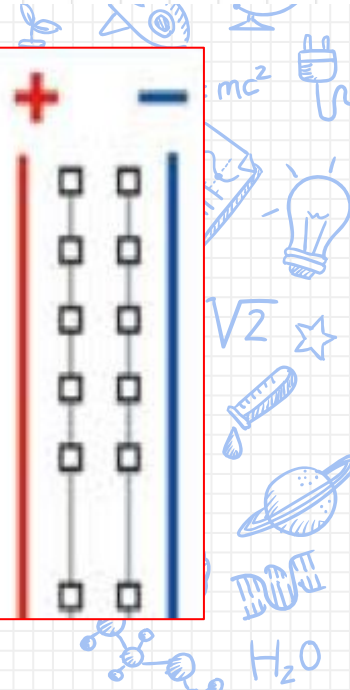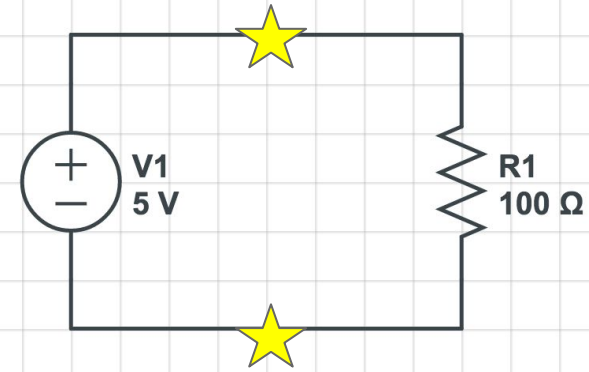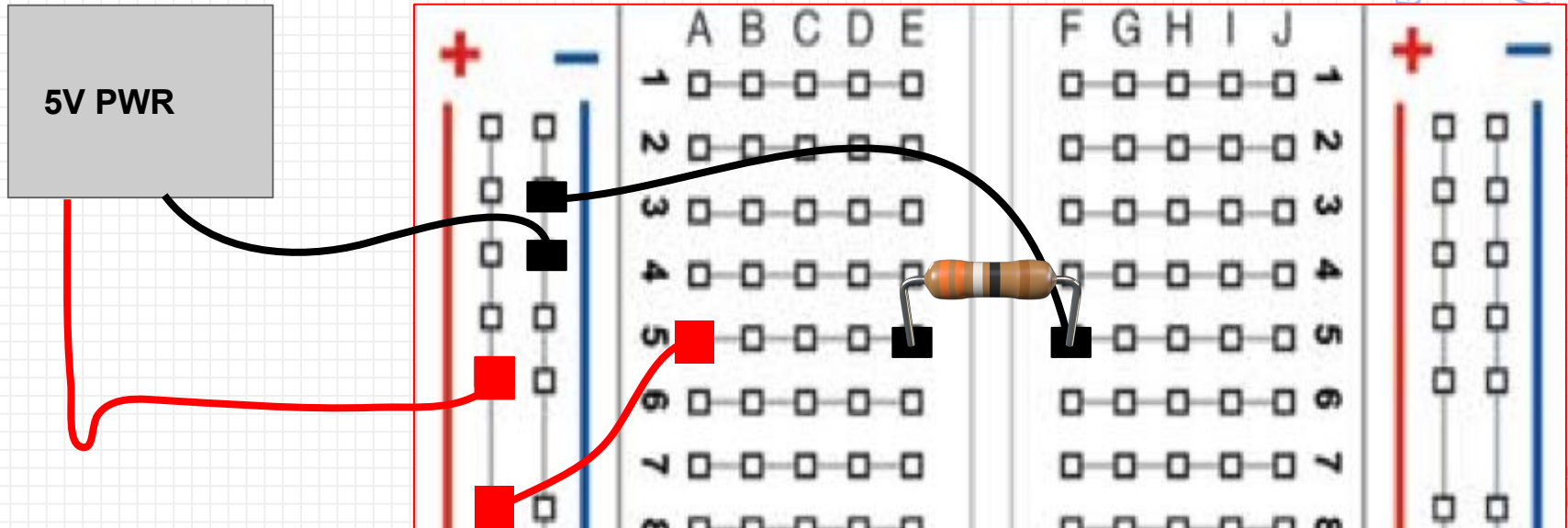- ✓ **Do** plug components across the gap in your breadboard - A-E and F-J are separate





Breadboard Do's and Don't's

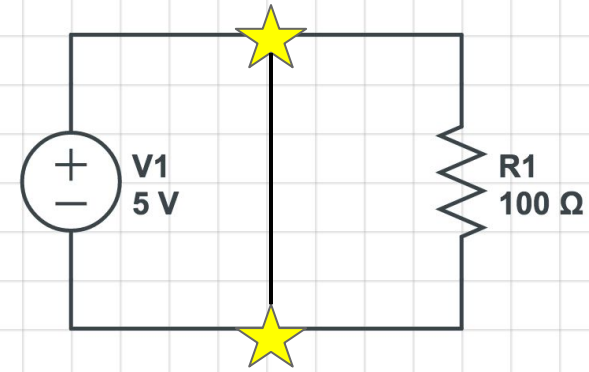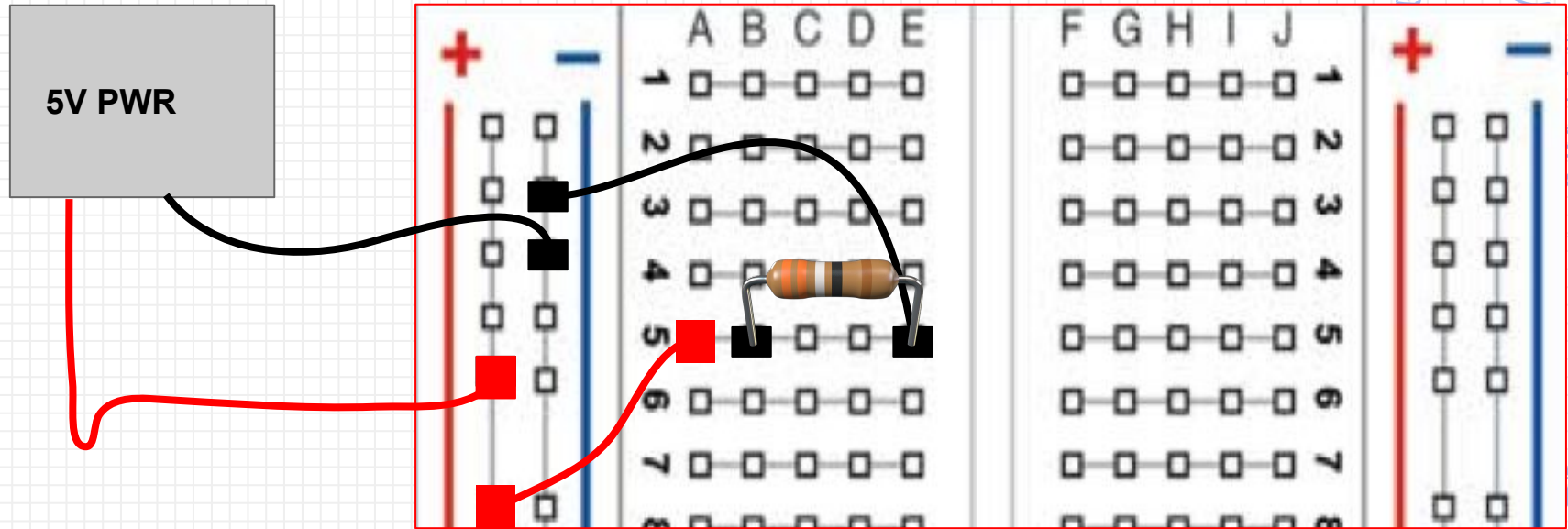Is this okay? If there is an error, where?





Breadboard Do's and Don't's

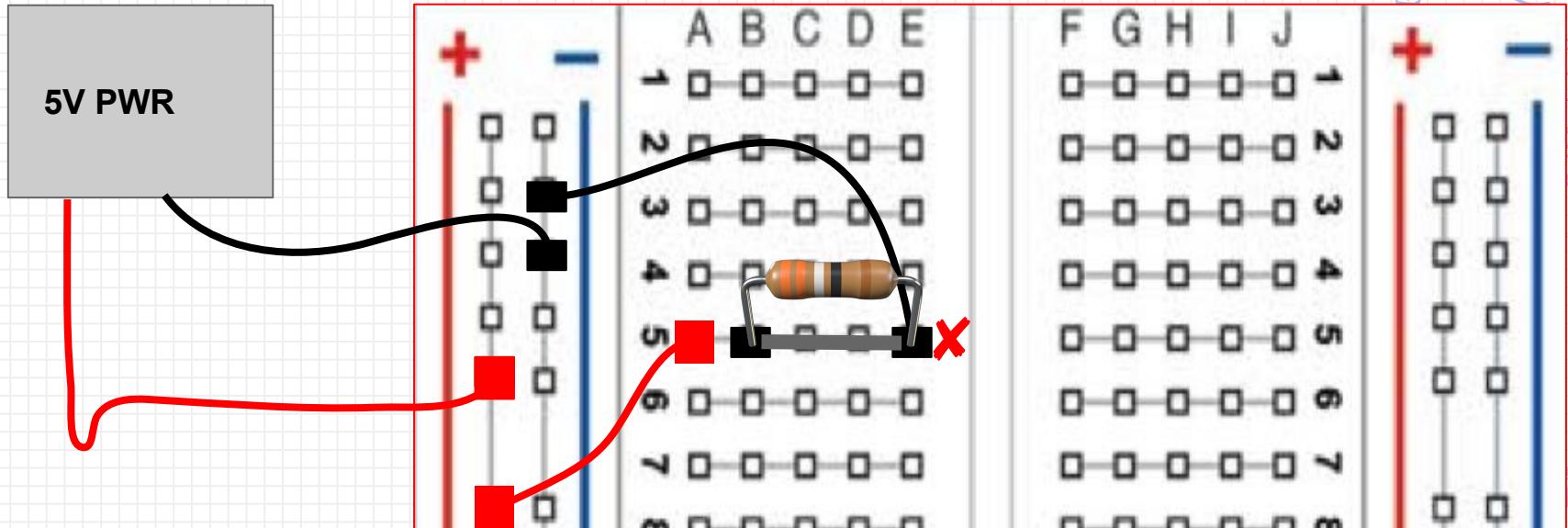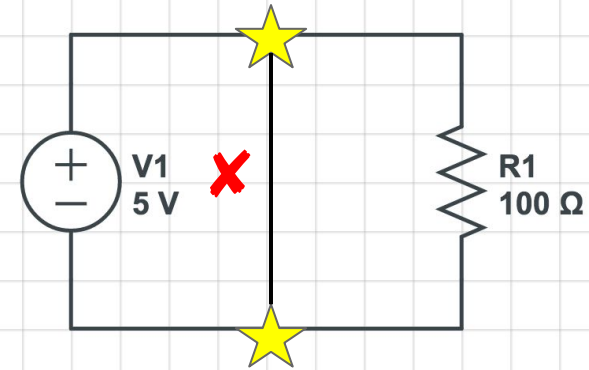✗ **Do not** plug both ends of component into the same row! This creates a short



Light-detecting Circuit

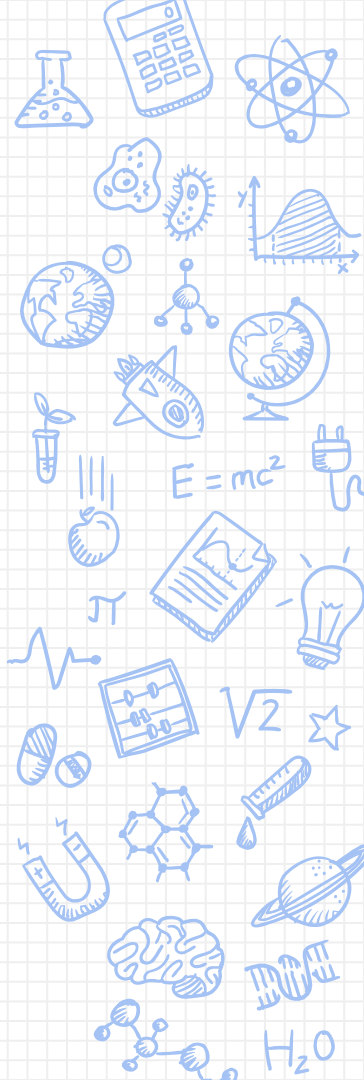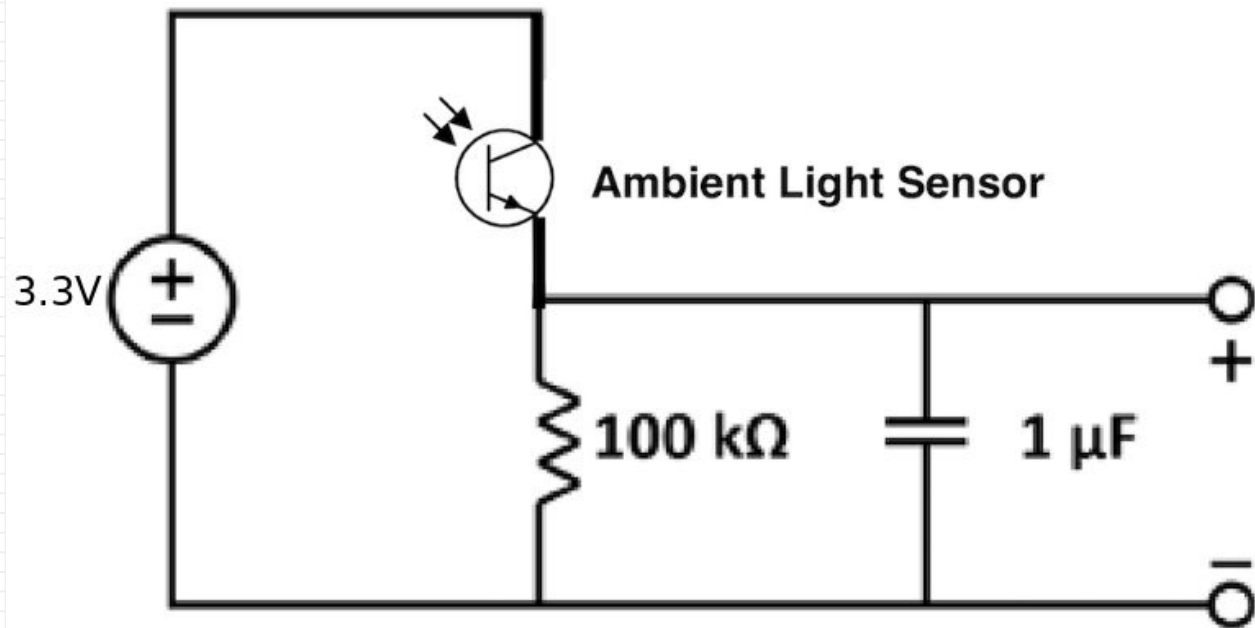

How to start

- Please use the station desktops for this lab
- If you need an instructional account, let us know
- Work in pairs
- This week's lab is listed as "Imaging Lab 1"
- **Make sure website says Spring 2020**

Wk	Date	Lecture Topic	Section	Lab	Homework
1	01/19 Tu	Introduction to Class: Welcome to EE16A! (Slides)	Section 0A	Installation Get Started: iPython + NumPy	Homework 0
	01/21 Th	Intro to Imaging/Tomography (Slides) (Notes)	Section 0B: dia0B.pdf		
2	01/26 Tu	Vectors and Systems of Equations (Notes)	Section 1A: TBA	Get Started: Lab Equipment	Homework 1
	01/28 Th	Linear Dependence	Section 1B: TBA		
3	02/02 Tu	Matrices and Transformations	Section 2A: TBA	Imaging Lab 1: Building a Light Sensor	Homework 2
	02/04 Th	Rank and Inverses	Section 2B: TBA		
4	02/09 Tu	Vector Spaces	Section 3A: TBA	Imaging Lab 2: Single Pixel Scanning	Homework 3
	02/11 Th	Nullspaces and Flows	Section 3B: TBA		
5	02/16 Tu	Special	Section 4A: Midterm review (no worksheet)	Buffer Week	Homework 4
Midterm					

- Lab notebook link is on course website
- Check following slide for common Energia Install errors and possible fixes
- Keep voltage source leads from LaunchPad to breadboard disconnected whilst building your circuit
 - Female ends can stay connected to the LaunchPad
- **Make sure you are using the correct resistors (Brown Black Yellow Gold for light sensor)**
- **Make sure your ambient light sensor is in the right direction**
- Complete the lab in **GROUPS OF 4** in your assigned breakout room
 - You must each build your own setup and answer all questions in your own notebook
- **DON'T LEAVE/PACK UP YOUR CIRCUIT WITHOUT BEING CHECKED OFF FIRST**
- Use the help queue and google checkoff form (linked in the lab)
 - lab.eecs16a.org

Common Energia Install Errors

- ✗ **Error:** The system cannot find the file specified
 - ✗ Fix: Manually update your board from version 1.0.6 to 1.0.7 (Tools --> Board --> Boards Manager --> Energia MSP430 Boards --> Update)
- ✗ **Error:** Serial monitor not displaying anything
 - ✗ Fix: select correct Baud rate in the serial monitor window (refer to lab notebook); press RST (reset) button on LaunchPad
- ✗ **Error:** Serial monitor displaying strange symbols
 - ✗ Fix: close serial monitor; reupload the code to the other COM port and open serial monitor again.
- ✗ **Error:** not detecting the launchpad as a launchpad (something like COM3 and COM4 show up)
 - ✗ Fix: if on Windows, make sure to install drivers <https://energia.nu/guide/install/windows/>
- ✗ **Error:** If you have a space in your Windows username and you encounter an error when running the program, follow these instructions (courtesy of a 16B student's Piazza post)
 - ✗ Energia stores some important stuff in this directory `C:\Users\First Last\AppData\Local\Energia15` - note: username has a space
 - ✗ Create the following directory structure: `C:\Users\First\AppData\Local`
 - ✗ Now copy the Energia15 folder from your actual home directory into the local folder in your firstname only user home directory.

