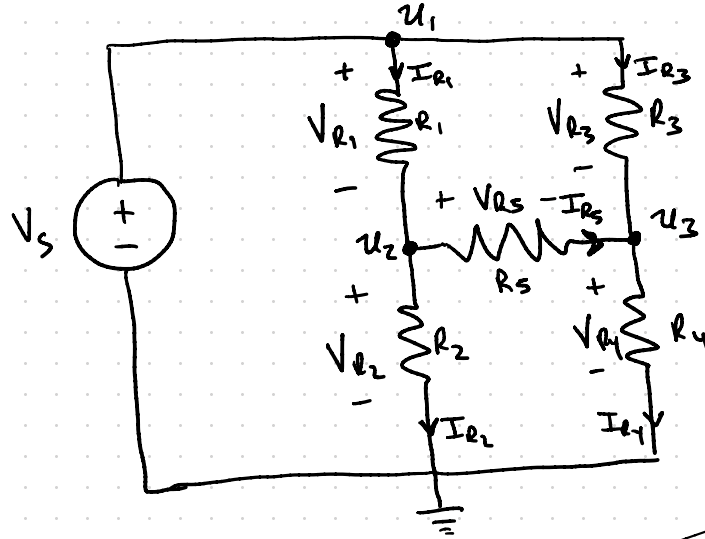


Steps of NVA

- 1) Define/label a reference node
- 2) Label all nodes whose voltage is set by a voltage source
- 3) Label all other nodes
- 4) Label all element voltages and currents following the "passive sign convention"
- 5) Write KCL expressions for all nodes with unknown voltages.
- 6) Substitute ^{element} Voltages and resistances for the currents in step 5
(using Ohm's Law)
- 7) Substitute node voltages for element voltages
- 8) Solve system for unknown node voltages



Q: Find all unknown node voltages

$$u_1 = V_S$$

KCL for u_2 : $I_{R_1} = I_{R_2} + I_{R_5}$

KCL for u_3 : $I_{R_5} + I_{R_3} = I_{R_4}$

$$\frac{V_{R_1}}{R_1} = \frac{V_{R_2}}{R_2} + \frac{V_{R_5}}{R_5}$$

$$\frac{V_{R_5}}{R_5} + \frac{V_{R_3}}{R_3} = \frac{V_{R_4}}{R_4}$$

$$\frac{u_1 - u_2}{R_1} = \frac{u_2}{R_2} + \frac{u_2 - u_3}{R_5}$$

$$\frac{u_2 - u_3}{R_5} + \frac{u_1 - u_3}{R_3} = \frac{u_3}{R_4}$$

$$V_s = 5 \text{ V}$$

$$R_1 = 1 \Omega$$

$$R_2 = 2 \Omega$$

$$R_3 = 3 \Omega$$

$$R_4 = 4 \Omega$$

$$R_5 = 5 \Omega$$

$$\frac{u_1 - u_2}{R_1} = \frac{u_2}{R_2} + \frac{u_2 - u_3}{R_5}$$

$$\frac{u_2 - u_3}{R_5} + \frac{u_1 - u_3}{R_3} = \frac{u_3}{R_4} \Rightarrow \frac{u_2}{5} + \frac{5}{3} = \frac{u_3}{4} + \frac{u_3}{5} + \frac{u_3}{3}$$

↑
solve for u_3


$$\Rightarrow \left(\frac{u_2}{5} + \frac{5}{3} \right) \left(\frac{1}{4} + \frac{1}{5} + \frac{1}{3} \right)^{-1} = u_3$$

$$\left(\frac{u_2}{5} + \frac{5}{3} \right) (1.276596) = u_3$$

then substitute
for u_3

$$u_2 \approx 3.31 \text{ V (ish)}$$

$$u_3 \approx 2.98 \text{ V (ish)}$$

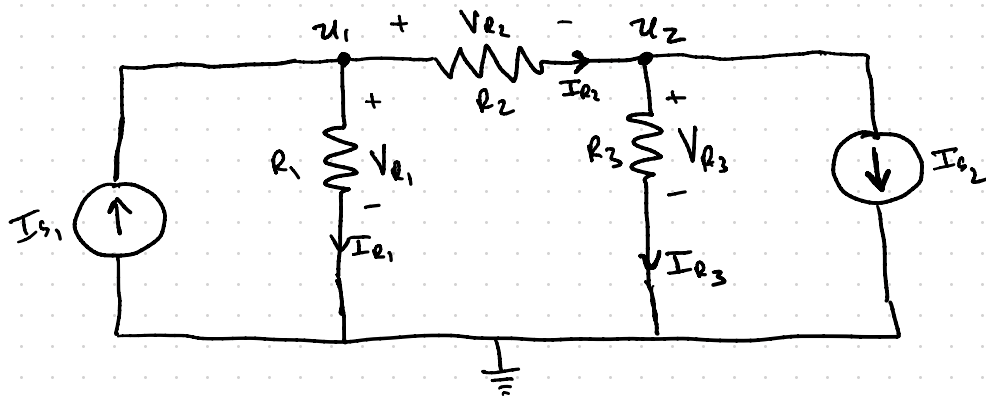

KCL for u_1 : $I_{s1} = I_{e1} + I_{e2} \Rightarrow 1 = I_{e1} + I_{e2} \Rightarrow 1 = \frac{V_{e1}}{R_1} + \frac{V_{e2}}{R_2}$

KCL for u_2 : $I_{e2} = I_{e3} + I_{s2} \Rightarrow 3 = I_{e2} - I_{e3} \Rightarrow 3 = \frac{V_{e2}}{R_2} - \frac{V_{e3}}{R_3}$

$$\left. \begin{aligned} 1 &= \frac{V_{e1}}{R_1} + \frac{V_{e2}}{R_2} \\ 3 &= \frac{V_{e2}}{R_2} - \frac{V_{e3}}{R_3} \end{aligned} \right\} \boxed{\begin{aligned} 1 &= \frac{u_1}{R_1} + \frac{u_1 - u_2}{R_2} \\ 3 &= \frac{u_1 - u_2}{R_2} - \frac{u_2}{R_3} \end{aligned}}$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ \frac{1}{R_2} & -\frac{1}{R_2} - \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 3 \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{10} + \frac{1}{20} & -\frac{1}{20} \\ \frac{1}{20} & -\frac{1}{20} - \frac{1}{50} \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 3 \end{bmatrix}$$

Solve for u_1, u_2 !


we found $u_1 = -10$, $u_2 = -50$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{u_1}{R_1} = \frac{-10}{10} = -1 \text{ A}$$

$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{-50}{50} = -1 \text{ A}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{u_1 - u_2}{R_2} = \frac{(-10 \text{ V}) - (-50 \text{ V})}{20 \Omega} = \frac{40 \text{ V}}{20 \Omega} = 2 \text{ A}$$

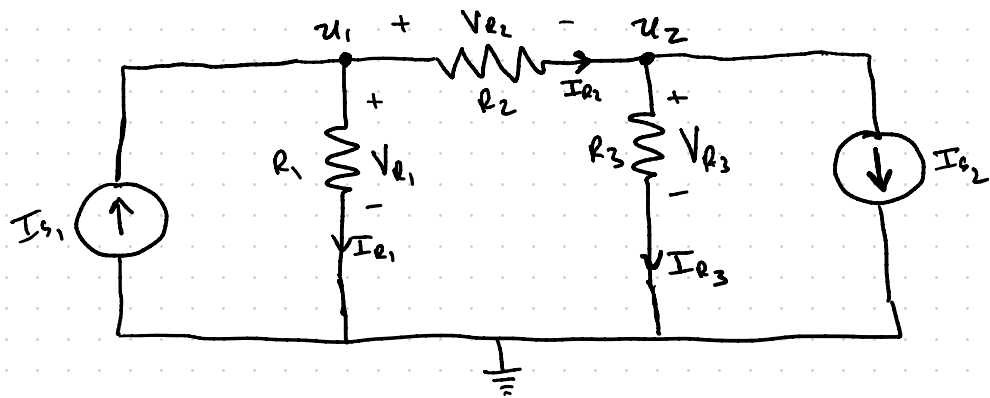Using Superposition to solve this... (on next page)



$$R_1 = 10 \Omega$$


$$R_2 = 20 \Omega$$

$$R_3 = 50 \Omega$$

$$I_{s1} = 1 \text{ A}$$

$$I_{s2} = 3 \text{ A}$$

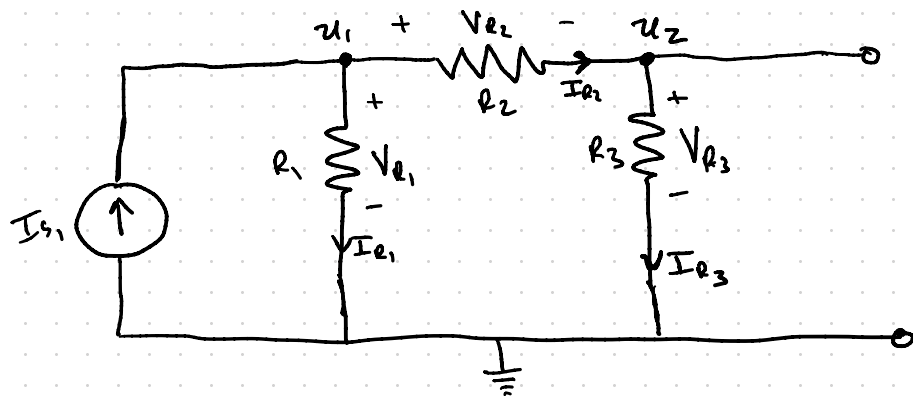Zeroing-out I_{s2} to solve for I_{s1} alone:



$$I_{s1} = I_{R1} + I_{R2}$$


$$1 = \frac{u_1}{10} + \frac{u_1 - u_2}{20}$$

$$u_2 = \frac{R_3}{R_2 + R_3} u_1 = \frac{5}{7} u_1$$

$$20 = 2u_1 + u_1 - \frac{5}{7}u_1$$

$$\Rightarrow 20 = \frac{10}{7} u_1 = u_1 = \frac{70}{8}$$

$$u_2 = \frac{50}{8}$$

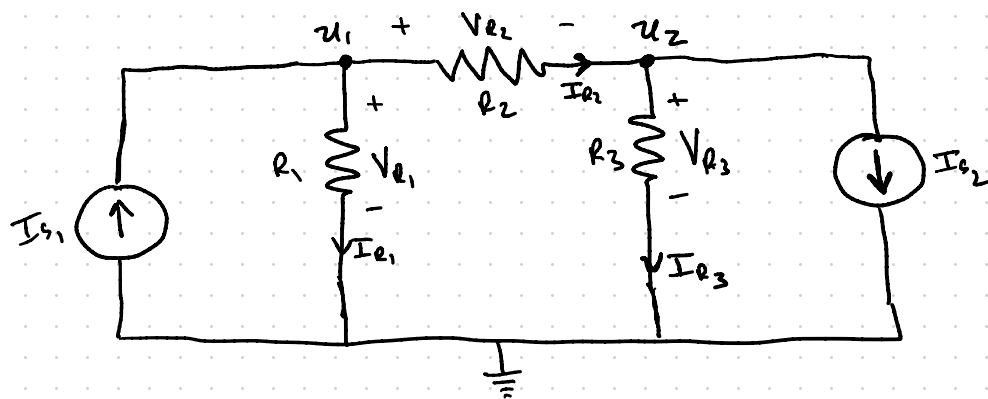

$$R_1 = 10 \Omega$$


$$R_2 = 20 \Omega$$

$$R_3 = 50 \Omega$$

$$I_{s1} = 1 \text{ A}$$

$$I_{s2} = 3 \text{ A}$$

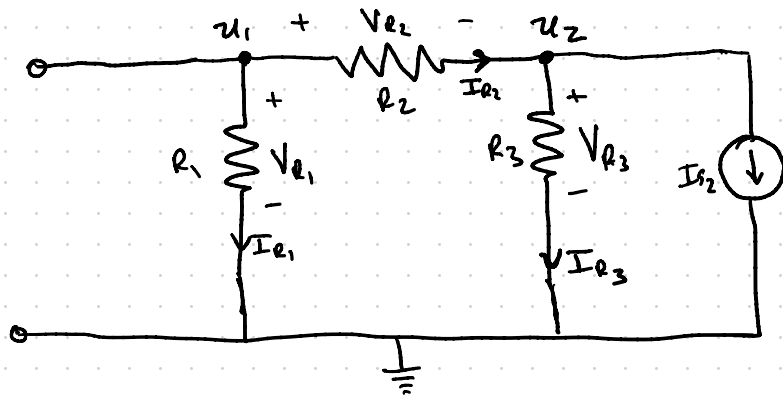Zeroing-out I_{s1} to solve for I_{s2} alone:



$$I_{s3} = I_{R2} - I_{R3}$$

$$3 = \frac{u_1 - u_2}{R_2} - \frac{u_2}{R_3} = \frac{u_1}{20} - \frac{u_2}{20} - \frac{u_2}{50} = \frac{u_1}{20} - \frac{7}{100} u_2$$

Also

$$u_1 = \frac{R_1}{R_1 + R_2} u_2 = \frac{1}{3} u_2 \Rightarrow u_2 = 3u_1$$

$$3 = \frac{u_1}{20} - \frac{7}{100} (3u_1)$$

$$= \left(\frac{5}{100} - \frac{21}{100} \right) u_1 \Rightarrow u_1 = \frac{-300}{16} = -\frac{150}{8}$$

$$\Rightarrow u_2 = -\frac{450}{8}$$

Putting the two cases together...

Just I_{c1}

$$u_1 = \frac{70}{8}$$

$$u_2 = \frac{50}{80}$$

Just I_{c2}

$$u_1 = -\frac{150}{8}$$

$$u_2 = -\frac{450}{8}$$

$$u_1 = \frac{70}{8} - \frac{150}{8} = -\frac{80}{8} = -10$$

$$u_2 = \frac{50}{8} - \frac{450}{8} = -\frac{400}{8} = -50$$

